

- Preface p. ix
- Survey of Electronics p. xiv
- S-1 A Brief History of the Development of Electronics p. 2
- S-2 Radio and Television Broadcasting p. 3
- S-3 Career Opportunities in Electronics p. 5
- S-4 A Preview of the Most Common Electronic Components p. 7
- S-5 Tools of the Trade p. 13
- Chapter 1 Electricity p. 14
- 1-1 Negative and Positive Polarities p. 16
- 1-2 Electrons and Protons in the Atom p. 16
- 1-3 Structure of the Atom p. 19
- 1-4 The Coulomb Unit of Electric Charge p. 22
- 1-5 The Volt Unit of Potential Difference p. 25
- 1-6 Charge in Motion Is Current p. 27
- 1-7 Resistance Is Opposition to Current p. 32
- 1-8 The Closed Circuit p. 34
- 1-9 Direction of the Current p. 36
- 1-10 Direct Current (DC) and Alternating Current (AC) p. 38
- 1-11 Sources of Electricity p. 39
- Summary and Review p. 41
- Chapter 2 Resistors p. 46
- 2-1 Types of Resistors p. 48
- 2-2 Resistor Color Coding p. 50
- 2-3 Variable Resistors p. 54
- 2-4 Rheostats and Potentiometers p. 56
- 2-5 Power Rating of Resistors p. 58
- 2-6 Series and Parallel Combinations of Resistors p. 59
- 2-7 Resistor Troubles p. 60
- Summary and Review p. 62
- Chapter 3 Ohm's Law p. 68
- 3-1 The Current $I = V/R$ p. 70
- 3-2 The Voltage $V = IR$ p. 73
- 3-3 The Resistance $R = V/I$ p. 73
- 3-4 Practical Units p. 74
- 3-5 Multiple Units p. 75
- 3-6 The Linear Proportion between V and I p. 76
- 3-7 Electric Power p. 78
- 3-8 Power Dissipation in Resistance p. 81
- 3-9 Power Formulas p. 84
- 3-10 Choosing the Resistor for a Circuit p. 86
- 3-11 Electric Shock p. 88
- 3-12 Open-Circuit and Short-Circuit Troubles p. 89
- 4-2 Total R Equals the Sum of All Series Resistances p. 100
- Summary and Review p. 90
- Chapter 4 Series Circuits p. 96
- 4-1 Why I Is the Same in All Parts of a Series Circuit p. 98

- 4-3 Series IR Voltage Drops p. 102
- 4-4 The Sum of Series IR Drops Equals the Applied $V_{[subscript T]}$ p. 103
- 4-5 Polarity of IR Voltage Drops p. 105
- 4-6 Total Power in a Series Circuit p. 106
- 4-7 Series-Aiding and Series-Opposing Voltages p. 107
- 4-8 Analyzing Series Circuits p. 108
- 4-9 Effect of an Open Circuit in a Series Path p. 110
- 4-10 Series Switches Represent the and Logic Function p. 112
- Summary and Review p. 114
- Chapter 5 Parallel Circuits p. 120
- 5-1 The Applied Voltage $V_{[subscript A]}$ Is the Same across Parallel Branches p. 122
- 5-2 Each Branch I Equals $V_{[subscript A]}/R$ p. 123
- 5-3 The Main-Line $I_{[subscript T]}$ Equals the Sum of the Branch Currents p. 124
- 5-4 Resistance in Parallel p. 127
- 5-5 Conductances in Parallel p. 133
- 5-6 Total Power in Parallel Circuits p. 134
- 5-7 Analyzing Parallel Circuits p. 135
- 5-8 Effect of an Open Branch in Parallel Circuits p. 136
- 5-9 Effect of a Short Circuit across Parallel Branches p. 137
- 5-10 Parallel Switches Represent the or Logic Function p. 138
- Summary and Review p. 140
- Chapter 6 Series-Parallel Circuits p. 146
- 6-1 Finding $R_{[subscript T]}$ for Series-Parallel Resistances p. 148
- 6-2 Resistance Strings in Parallel p. 149
- 6-3 Resistance Banks in Series p. 151
- 6-4 Resistance Banks and Strings in Series-Parallel p. 153
- 6-5 Analyzing Series-Parallel Circuits p. 155
- 6-6 Wheatstone Bridge p. 158
- 6-7 Chassis-Ground Connections p. 159
- 6-8 Voltages Measured to Chassis Ground p. 160
- 6-9 Opens and Shorts in Series-Parallel Circuits p. 163
- 6-10 Series-Parallel Switches Combine the and and or Logic Functions p. 164
- Summary and Review p. 166
- Review: Chapters 1 To 6 p. 173
- Chapter 7 Voltage Dividers and Current Dividers p. 176
- 7-1 Series Voltage Dividers p. 178
- 7-2 Current Divider with Two Parallel Resistances p. 180
- 7-3 Current Division by Parallel Conductances p. 183
- 7-4 Series Voltage Divider with Parallel Load Current p. 184
- 7-5 Design of a Loaded Voltage Divider p. 186
- Summary and Review p. 189
- Chapter 8 Direct-Current Meters p. 194
- 8-1 Moving-Coil Meter p. 196
- 8-2 Measurement of Current p. 198
- 8-3 Meter Shunts p. 200
- 8-4 Voltmeters p. 203

- 8-5 Loading Effect of a Voltmeter p. 208
- 8-6 Ohmmeters p. 210
- 8-7 Multimeters p. 214
- 8-8 Digital Multimeter (DMM) p. 217
- 8-9 Meter Applications p. 219
- 8-10 Checking Continuity with the Ohmmeter p. 222
- Summary and Review p. 224
- Review: Chapters 7 And 8 p. 230
- Chapter 9 Kirchhoff's Laws p. 232
- 9-1 Kirchhoff's Current Law (KCL) p. 234
- 9-2 Kirchhoff's Voltage Law (KVL) p. 235
- 9-3 Method of Branch Currents p. 237
- 9-4 Node-Voltage Analysis p. 241
- 9-5 Method of Mesh Currents p. 244
- Summary and Review p. 248
- Chapter 10 Network Theorems p. 252
- 10-1 Superposition p. 254
- 10-2 Thevenin's Theorem p. 256
- 10-3 Thevenizing a Circuit with Two Voltage Sources p. 259
- 10-4 Thevenizing a Bridge Circuit p. 260
- 10-5 Norton's Theorem p. 262
- 10-6 Thevenin-Norton Conversions p. 266
- 10-7 Conversion of Voltage and Current Sources p. 268
- 10-8 Millman's Theorem p. 270
- Review: Chapters 9 and 10 p. 286
- 10-9 Circuits with Current Sources p. 272
- 10-10 T or Y and π or Δ Connections p. 275
- Summary and Review p. 280
- Chapter 11 Conductors and Insulators p. 288
- 11-1 Function of the Conductor p. 290
- 11-2 Standard Wire Gage Sizes p. 290
- 11-3 Types of Wire Conductors p. 293
- 11-4 Connectors p. 295
- 11-5 Printed Wiring p. 296
- 11-6 Switches p. 297
- 11-7 Fuses p. 299
- 11-8 Wire Resistance p. 301
- 11-9 Temperature Coefficient of Resistance p. 304
- 11-10 Ion Current in Liquids and Gases p. 306
- 11-11 Electrons and Hole Charges in Semiconductors p. 308
- 11-12 Insulators p. 310
- 11-13 Troubleshooting Hints for Wires and Connectors p. 311
- Summary and Review p. 313
- Chapter 12 Batteries p. 318
- 12-1 General Features of Batteries p. 320
- 12-2 The Voltaic Cell p. 322

- 12-3 Carbon-Zinc Dry Cell p. 324
- 12-4 Alkaline Cell p. 325
- 12-5 Additional Types of Primary Cells p. 327
- 12-6 Summary of Dry Cells p. 328
- 12-7 Lithium Cell p. 329
- 12-8 Lead-Acid Wet Cell p. 330
- 12-9 Additional Types of Secondary Cells p. 334
- 12-10 Series and Parallel Cells p. 336
- 12-11 Current Drain Depends on Load Resistance p. 338
- 12-12 Internal Resistance of a Generator p. 339
- Summary and Review p. 346
- 12-13 Why the Terminal Voltage Drops with More Load Current p. 340
- 12-14 Constant-Voltage and Constant-Current Sources p. 343
- 12-15 Matching a Load Resistance to the Generator r_i p. 343
- Review: Chapters 11 and 12 p. 350
- Chapter 13 Magnetism p. 352
- 13-1 The Magnetic Field ϕ p. 354
- 13-2 Magnetic Flux μ p. 355
- 13-3 Flux Density B p. 357
- 13-4 Induction by the Magnetic Field p. 360
- 13-5 Air Gap of a Magnet p. 361
- 13-6 Types of Magnets p. 362
- 13-7 Ferrites p. 364
- 13-8 Magnetic Shielding p. 365
- 13-9 The Hall Effect p. 366
- Summary and Review p. 367
- Chapter 14 Magnetic Units p. 370
- 14-1 Ampere-Turns of Magnetomotive Force (mmf) p. 372
- 14-2 Field Intensity (H) p. 373
- 14-3 Permeability (μ) p. 375
- 14-4 B-H Magnetization Curve p. 377
- 14-5 Magnetic Hysteresis p. 378
- 14-6 Ohm's Law for Magnetic Circuits p. 380
- 14-7 Relations between Magnetic Units p. 382
- 14-8 Comparison of Magnetic and Electric Fields p. 383
- Summary and Review p. 386
- Chapter 15 Electromagnetic Induction p. 390
- 15-1 Magnetic Field around an Electric Current p. 392
- 15-2 Magnetic Polarity of a Coil p. 394
- 15-3 Motor Action between Two Magnetic Fields p. 395
- 15-4 Induced Current p. 398
- 15-5 Lenz' Law p. 399
- 15-6 Generating an Induced Voltage p. 400
- 15-7 Faraday's Law of Induced Voltage p. 402
- 15-8 Relays p. 404
- Summary and Review p. 408

- Chapter 16 Alternating Voltage and Current p. 414
- 16-1 Alternating Current Applications p. 416
- 16-2 Alternating-Voltage Generator p. 417
- 16-3 The Sine Wave p. 420
- 16-4 Alternating Current p. 423
- 16-5 Voltage and Current Values for a Sine Wave p. 424
- 16-6 Frequency p. 427
- 16-7 Period p. 428
- 16-8 Wavelength p. 430
- 16-9 Phase Angle p. 423
- 16-10 The Time Factor in Frequency and Phase p. 436
- 16-11 Alternating Current Circuits with Resistance p. 437
- 16-12 Nonsinusoidal AC Waveforms p. 440
- 16-13 Harmonic Frequencies p. 442
- 16-14 The 60-Hz AC Power Line p. 442
- 16-15 Motors and Generators p. 445
- 16-16 Three-Phase AC Power p. 447
- Summary and Review p. 450
- Review: Chapters 13 to 16 p. 456
- Chapter 17 Capacitance p. 458
- 17-1 How Charge Is Stored in the Dielectric p. 460
- 17-2 Charging and Discharging a Capacitor p. 461
- 17-3 The Farad Unit of Capacitance p. 463
- 17-4 Typical Capacitors p. 468
- 17-5 Electrolytic Capacitors p. 472
- 17-6 Capacitor Coding p. 474
- 17-7 Parallel Capacitances p. 481
- 17-8 Series Capacitances p. 481
- 17-9 Stray Capacitive and Inductive Effects p. 483
- 17-10 Energy in Electrostatic Field of Capacitance p. 485
- 17-11 Troubles in Capacitors p. 487
- 18-2 The Amount of X_C Equals $1/(2\pi fC)$ p. 499
- Summary and Review p. 490
- Chapter 18 Capacitive Reactance p. 496
- 18-1 Alternating Current in a Capacitive Circuit p. 498
- 18-3 Series or Parallel Capacitive Reactances p. 503
- 18-4 Ohm's Law Applied to X_C p. 504
- 18-5 Applications of Capacitive Reactance p. 505
- 18-6 Sine-Wave Charge and Discharge Current p. 506
- Summary and Review p. 511
- Chapter 19 Capacitive Circuits p. 516
- 19-1 Sine-Wave v_C Lags i_C by 90° p. 518
- 19-2 X_C and R in Series p. 519
- 19-3 RC Phase-Shifter Circuit p. 522
- 19-4 X_C and R in Parallel p. 524
- 19-5 RF and AF Coupling Capacitors p. 527

- 19-6 Capacitive Voltage Dividers p. 528
- 19-7 The General Case of Capacitive Current i_C p. 530
- Summary and Review p. 531
- Review: Chapters 17 to 19 p. 537
- Chapter 20 Inductance p. 540
- 20-1 Induction by Alternating Current p. 542
- 20-2 Self-Inductance L p. 543
- 20-3 Self-Induced Voltage v_L p. 546
- 20-4 How v_L Opposes a Change in Current p. 547
- 20-5 Mutual Inductance M p. 548
- 20-6 Transformers p. 552
- 20-7 Transformer Ratings p. 558
- 20-8 Impedance Transformation p. 563
- 20-9 Core Losses p. 567
- 20-10 Types of Cores p. 568
- 20-11 Variable Inductance p. 569
- 20-12 Inductances in Series or Parallel p. 570
- 20-13 Stray Inductance p. 573
- 20-14 Energy in Magnetic Field of Inductance p. 573
- 20-15 Troubles in Coils p. 575
- Summary and Review p. 577
- Chapter 21 Inductive Reactance p. 584
- 21-1 How X_L Reduces the Amount of I p. 586
- 21-2 $X_L = 2\pi fL$ p. 587
- 21-3 Series or Parallel Inductive Reactances p. 591
- Summary and Review p. 599
- 21-4 Ohm's Law Applied to X_L p. 592
- 21-5 Applications of X_L for Different Frequencies p. 593
- 21-6 Waveshape of v_L Induced by Sine-Wave Current p. 594
- Chapter 22 Inductive Circuits p. 604
- 22-1 Sine-Wave i_L Lags v_L by 90° p. 606
- 22-2 X_L and R in Series p. 607
- 22-3 Impedance Z Triangle p. 610
- 22-4 X_L and R in Parallel p. 613
- 22-5 Q of a Coil p. 617
- 22-6 AF and RF Chokes p. 619
- 22-7 The General Case of Inductive Voltage p. 621
- Summary and Review p. 624
- Chapter 23 R_C and L/R Time Constants p. 630
- 23-1 Response of Resistance Alone p. 632
- 23-2 L/R Time Constant p. 632
- 23-3 High Voltage Produced by Opening an RL Circuit p. 634
- 23-4 RC Time Constant p. 636
- 23-5 RC Charge and Discharge Curves p. 639
- 23-6 High Current Produced by Short-circuiting RC Circuit p. 640
- 23-7 RC Waveshapes p. 642

- 23-8 Long and Short Time Constants p. 644
- 23-9 Charge and Discharge with Short RC Time Constant p. 645
- 23-10 Long Time Constant for RC Coupling Circuit p. 647
- 23-11 Universal Time Constant Graph p. 648
- 23-12 Comparison of Reactance and Time Constant p. 653
- Summary and Review p. 655
- Review: Chapters 20 to 23 p. 661
- Chapter 24 Alternating Current Circuits p. 664
- 24-1 AC Circuits with Resistance but No Reactance p. 666
- 24-2 Circuits with X_L Alone p. 667
- 24-3 Circuits with X_C Alone p. 668
- 24-4 Opposite Reactances Cancel p. 669
- 24-5 Series Reactance and Resistance p. 671
- 24-6 Parallel Reactance and Resistance p. 674
- 24-7 Series-Parallel Reactance and Resistance p. 676
- 24-8 Real Power p. 677
- 24-9 AC Meters p. 680
- 24-10 Wattmeters p. 681
- 24-11 Summary of Types of Ohms in AC Circuits p. 682
- 24-12 Summary of Types of Phasors in AC Circuits p. 683
- Summary and Review p. 686
- Chapter 25 Complex Numbers for AC Circuits p. 690
- 25-1 Positive and Negative Numbers p. 692
- 25-2 The j Operator p. 692
- 25-3 Definition of a Complex Number p. 694
- 25-4 How Complex Numbers Are Applied to AC Circuits p. 695
- 25-5 Impedance in Complex Form p. 696
- 25-6 Operations with Complex Numbers p. 698
- 25-7 Magnitude and Angle of a Complex Number p. 700
- 25-8 Polar Form of Complex Numbers p. 701
- 25-9 Converting Polar to Rectangular Form p. 703
- 25-13 Combining Complex Branch Currents p. 711
- 25-10 Complex Numbers in Series AC Circuits p. 705
- 25-11 Complex Numbers in Parallel AC Circuits p. 708
- 25-12 Combining Two Complex Branch Impedances p. 710
- 25-14 Parallel Circuit with Three Complex Branches p. 712
- Summary and Review p. 715
- Review: Chapters 24 and 25 p. 720
- Chapter 26 Resonance p. 722
- 26-1 The Resonance Effect p. 724
- 26-2 Series Resonance p. 725
- 26-3 Parallel Resonance p. 728
- 26-4 Resonant Frequency $f_r = 1/(2\pi LC)$ p. 732
- 26-5 Q Magnification Factor of Resonant Circuit p. 736
- 26-6 Bandwidth of Resonant Circuit p. 740

- 26-7 Tuning p. 744
- 26-8 Mistuning p. 746
- 26-9 Analysis of Parallel Resonant Circuits p. 747
- 26-10 Damping of Parallel Resonant Circuits p. 749
- 26-11 Choosing L and C for a Resonant Circuit p. 751
- Summary and Review p. 752
- Chapter 27 Filters p. 758
- 27-1 Examples of Filtering p. 760
- 27-2 Direct Current Combined with Alternating Current p. 760
- 27-3 Transformer Coupling p. 763
- 27-4 Capacitive Coupling p. 764
- 27-5 Bypass Capacitors p. 767
- 27-6 Filter Circuits p. 770
- 27-7 Low-Pass Filters p. 771
- 27-8 High-Pass Filters p. 773
- 27-9 Analyzing Filter Circuits p. 774
- 27-10 Decibels and Frequency Response Curves p. 784
- 27-11 Resonant Filters p. 791
- Chapter 28 Electronic Devices p. 804
- 27-12 Interference Filters p. 794
- Summary and Review p. 795
- Review: Chapters 26 and 27 p. 801
- 28-1 Semiconductors p. 806
- 28-2 The PN Junction p. 811
- 28-3 Semiconductor Diodes p. 816
- 28-4 PNP and NPN Transistors p. 818
- 28-5 Field-Effect Transistor (FET) p. 823
- 28-6 Testing Diodes and Thyristors p. 827
- Summary and Review p. 830
- Chapter 29 Electronic Circuits p. 834
- 29-1 Analog and Digital Signals p. 836
- 29-2 Amplifier Gain p. 838
- 29-3 Characteristics of Amplifier Circuits p. 841
- 29-4 Oscillators p. 847
- 29-5 Multivibrators p. 850
- 29-6 Modulation p. 853
- 29-7 Diode Rectifiers p. 857
- 29-8 Troubleshooting the DC Supply Voltage p. 860
- Summary and Review p. 864
- Chapter 30 Transistor Amplifiers p. 868
- 30-1 Circuit Configurations p. 870
- 30-2 Class A, B, or C Operation p. 873
- 30-3 Analysis of Common-Emitter (CE) Amplifier p. 875
- 30-4 Collector Characteristic Curves p. 879
- 30-5 Letter Symbols for Transistors p. 881
- 30-6 FET Amplifiers p. 882

- 30-7 Troubleshooting Amplifier Circuits p. 884
- Summary and Review p. 888
- Review: Chapters 28 to 30 p. 890
- Chapter 31 Digital Electronics p. 892
- 31-1 Comparing Binary and Decimal Numbers p. 894
- 31-2 Decimal to Binary Conversion p. 896
- 31-3 Hexadecimal Numbers p. 896
- 31-4 Binary Coded Decimal System p. 900
- 31-5 The ASCII Code p. 901
- 31-6 Logic Gates, Symbols, and Truth Tables p. 902
- 31-7 Boolean Algebra p. 906
- 31-8 DeMorgan's Theorem p. 909
- 31-9 Active high/Active low Terminology p. 912
- 31-10 Treating Unused Inputs on Logic Gates p. 914
- 31-11 Combinational Logic Circuits p. 915
- 31-12 Flip-Flops p. 918
- 31-13 Binary Counters p. 922
- 31-14 New Logic Symbols p. 925
- Summary and Review p. 927
- Chapter 32 Integrated Circuits p. 932
- 32-1 Operational Amplifiers and Their Characteristics p. 934
- 32-2 Op Amp Circuits p. 941
- Summary and Review p. 950
- Review: Chapters 31 and 32 p. 953
- Appendix A Electrical Symbols and Abbreviations p. 955
- Appendix B Solder and the Soldering Process p. 957
- Appendix C Schematic Symbols p. 964
- Appendix D Using the Oscilloscope p. 966
- Glossary p. 981
- Answers to Self-Tests p. 988
- Answers to Odd-Numbered Problems and Critical Thinking Problems p. 992
- Index p. 1002