

- 1 Introduction to Analog Design
- 2 Basic MOS Device Physics
- 3 Single-Stage Amplifiers
- 4 Differential Amplifiers
- 5 Passive and Active Current Mirrors
- 6 Frequency Response of Amplifiers
- 7 Noise
- 8 Feedback
- 9 Operational Amplifiers
- 10 Stability and Frequency Compensation
- 11 Bandgap References
- 12 Introduction to Switched-Capacitor Circuits
- 13 Nonlinearity and Mismatch
- 14 Oscillators
- 15 Phase-Locked Loops
- 16 Short-Channel Effects and Device Models
- 17 CMOS Processing Technology
- 18 Layout and Packaging