

## Table of Contents

- Part I DC Circuits
- 1 Components, Quantities, and Units p. 2
- 1-1 Electrical Components and Measuring Instruments p. 4
- 1-2 Electrical and Magnetic Units p. 9
- 1-3 Scientific Notation p. 10
- 1-4 Engineering Notation and Metric Prefixes p. 15
- 1-5 Metric Unit Conversions p. 18
- 2 Voltage, Current, and Resistance in Electric Circuits p. 26
- 2-1 Atoms p. 28
- 2-2 Electrical Charge p. 32
- 2-3 Voltage p. 34
- 2-4 Current p. 37
- 2-5 Resistance p. 39
- 2-6 The Electric Circuit p. 48
- 2-7 Basic Circuit Measurements p. 55
- 2-8 Electrical Safety p. 62
- Application Assignment: Putting Your Knowledge to Work p. 65
- 3 Ohm's Law, Energy, and Power p. 78
- 3-1 Ohm's Law p. 80
- 3-2 Application of Ohm's Law p. 84
- 3-3 Energy and Power p. 90
- 3-4 Power in an Electric Circuit p. 93
- 3-5 The Power Rating of Resistors p. 96
- 3-6 Energy Conversion and Voltage Drop in a Resistance p. 100
- 3-7 Power Supplies p. 101
- 3-8 Introduction to Troubleshooting p. 103
- Application Assignment: Putting Your Knowledge to Work p. 106
- 4 Series Circuits p. 120
- 4-1 Resistors in Series p. 122
- 4-2 Current in a Series Circuit p. 124
- 4-3 Total Series Resistance p. 126
- 4-4 Ohm's Law in Series Circuits p. 130
- 4-5 Voltage Sources in Series p. 135
- 4-6 Kirchhoff's Voltage Law p. 137
- 4-7 Voltage Dividers p. 141
- 4-8 Power in a Series Circuit p. 148
- 4-9 Circuit Ground p. 150
- 4-10 Troubleshooting p. 154
- Application Assignment: Putting Your Knowledge to Work p. 158
- 5 Parallel Circuits p. 174
- 5-1 Resistors in Parallel p. 176
- 5-2 Voltage in Parallel Circuits p. 179
- 5-3 Kirchhoff's Current Law p. 180
- 5-4 Total Parallel Resistance p. 184

- 5-5 Ohm's Law in Parallel Circuits p. 191
- 5-6 Current Dividers p. 195
- 5-7 Power in Parallel Circuits p. 199
- 5-8 Troubleshooting p. 201
- Application Assignment: Putting Your Knowledge to Work p. 205
- 6 Series-Parallel Circuits p. 222
- 6-1 Identifying Series-Parallel Relationships p. 224
- 6-2 Analysis of Series-Parallel Circuits p. 229
- 6-3 Voltage Dividers with Resistive Loads p. 237
- 6-4 Loading Effect of a Voltmeter p. 242
- 6-5 The Wheatstone Bridge p. 245
- 6-6 Thevenin's Theorem p. 250
- 6-7 The Superposition Theorem p. 262
- 6-8 Troubleshooting p. 264
- Application Assignment: Putting Your Knowledge to Work p. 269
- 7 Magnetism and Electromagnetism p. 288
- 7-1 The Magnetic Field p. 290
- 7-2 Electromagnetism p. 294
- 7-3 Electromagnetic Devices p. 300
- 7-4 Magnetic Hysteresis p. 304
- 7-5 Electromagnetic Induction p. 306
- 7-6 Applications of Electromagnetic Induction p. 310
- Application Assignment: Putting Your Knowledge to Work p. 314
- Part II AC Circuits
- 8 Introduction to Alternating Current and Voltage p. 324
- 8-1 The Sine Wave p. 326
- 8-2 Sinusoidal Voltage Sources p. 331
- 8-3 Voltage and Current Values of Sine Waves p. 335
- 8-4 Angular Measurement of a Sine Wave p. 339
- 8-5 The Sine Wave Formula p. 343
- 8-6 Ohm's Law and Kirchhoff's Laws in AC Circuits p. 346
- 8-7 Superimposed DC and AC Voltages p. 348
- 8-8 Nonsinusoidal Waveforms p. 350
- 8-9 The Oscilloscope p. 357
- Application Assignment: Putting Your Knowledge to Work p. 364
- 9 Capacitors p. 380
- 9-1 The Basic Capacitor p. 382
- 9-2 Types of Capacitors p. 389
- 9-3 Series Capacitors p. 395
- 9-4 Parallel Capacitors p. 399
- 9-5 Capacitors in DC Circuits p. 401
- 9-6 Capacitors in AC Circuits p. 409
- 9-7 Capacitor Applications p. 415
- 9-8 Testing Capacitors p. 419
- Application Assignment: Putting Your Knowledge to Work p. 422
- 10 RC Circuits p. 438

- 10-1 Sinusoidal Response of RC Circuits p. 440
- 10-2 Impedance and Phase Angle of Series RC Circuits p. 441
- 10-3 Analysis of Series RC Circuits p. 443
- 10-4 Impedance and Phase Angle of Parallel RC Circuits p. 450
- 10-5 Analysis of Parallel RC Circuits p. 453
- 10-6 Series-Parallel Analysis p. 458
- 10-7 Power in RC Circuits p. 463
- 10-8 Basic Applications p. 467
- 10-9 Troubleshooting p. 477
- Application Assignment: Putting Your Knowledge to Work p. 482
- 11 Inductors p. 500
- 11-1 The Basic Inductor p. 502
- 11-2 Types of Inductors p. 507
- 11-3 Series Inductors p. 508
- 11-4 Parallel Inductors p. 509
- 11-5 Inductors in DC Circuits p. 511
- 11-6 Inductors in AC Circuits p. 521
- 11-7 Inductor Applications p. 527
- 11-8 Testing Inductors p. 528
- Application Assignment: Putting Your Knowledge to Work p. 529
- 12 RL Circuits p. 540
- 12-1 Sinusoidal Response of RL Circuits p. 542
- 12-2 Impedance and Phase Angle of Series RL Circuits p. 543
- 12-3 Analysis of Series RL Circuits p. 545
- 12-4 Impedance and Phase Angle of Parallel RL Circuits p. 550
- 12-5 Analysis of Parallel RL Circuits p. 553
- 12-6 Series-Parallel Analysis p. 556
- 12-7 Power in RL Circuits p. 559
- 12-8 Basic Applications p. 563
- 12-9 Troubleshooting p. 569
- Application Assignment: Putting Your Knowledge to Work p. 574
- 13 RLC Circuits and Resonance p. 588
- 13-1 Impedance and Phase Angle of Series RLC Circuits p. 590
- 13-2 Analysis of Series RLC Circuits p. 591
- 13-3 Series Resonance p. 596
- 13-4 Series Resonant Filters p. 603
- 13-5 Parallel RLC Circuits p. 612
- 13-6 Parallel Resonance p. 617
- 13-7 Parallel Resonant Filters p. 625
- 13-8 Applications p. 631
- Application Assignment: Putting Your Knowledge to Work p. 634
- 14 Transformers p. 646
- 14-1 Mutual Inductance p. 648
- 14-2 The Basic Transformer p. 649
- 14-3 Step-Up Transformers p. 653
- 14-4 Step-Down Transformers p. 654

- 14-5 Loading the Secondary p. 655
- 14-6 Reflected Load p. 657
- 14-7 Matching the Load and Source Resistances p. 660
- 14-8 The Transformer as an Isolation Device p. 663
- 14-9 Nonideal Transformer Characteristics p. 664
- 14-10 Other Types of Transformers p. 667
- 14-11 Troubleshooting p. 671
- Application Assignment: Putting Your Knowledge to Work p. 674
- 15 Pulse Response of Reactive Circuits p. 686
- 15-1 The RC Integrator p. 688
- 15-2 Single-Pulse Response of RC Integrators p. 689
- 15-3 Repetitive-Pulse Response of RC Integrators p. 694
- 15-4 Single-Pulse Response of RC Differentiators p. 699
- 15-5 Repetitive-Pulse Response of RC Differentiators p. 704
- 15-6 Pulse Response of RL Integrators p. 706
- 15-7 Pulse Response of RL Differentiators p. 711
- 15-8 Applications p. 715
- 15-9 Troubleshooting p. 718
- Application Assignment: Putting Your Knowledge to Work p. 720
- Part III Devices
- 16 Introduction to Semiconductors p. 734
- 16-1 Atomic Structure and Semiconductors p. 736
- 16-2 Atomic Bonding p. 737
- 16-3 Conduction in Semiconductors p. 739
- 16-7 Diode Characteristics p. 751
- 16-4 N-Type and P-Type Semiconductors p. 742
- 16-5 The PN Junction p. 744
- 16-6 Biasing the PN Junction p. 746
- Application Assignment: Putting Your Knowledge to Work p. 757
- 17 Diodes and Applications p. 768
- 17-1 Half-Wave Rectifiers p. 770
- 17-2 Full-Wave Rectifiers p. 774
- 17-3 Power Supply Filters and Regulators p. 780
- 17-4 Diode Limiting and Clamping Circuits p. 786
- 17-5 Zener Diodes p. 792
- 17-6 Varactor Diodes p. 800
- 17-7 LEDs and Photodiodes p. 802
- 17-8 The Diode Data Sheet p. 806
- 17-9 Troubleshooting p. 811
- Application Assignment: Putting Your Knowledge to Work p. 819
- 18 Transistors and Thyristors p. 834
- 18-1 Bipolar Junction Transistors (BJTs) p. 836
- 18-2 Voltage-Divider Bias p. 840
- 18-3 The Bipolar Junction Transistor as an Amplifier p. 842
- 18-4 The BJT as a Switch p. 849
- 18-5 BJT Parameters and Ratings p. 851

- 18-6 The Junction Field-Effect Transistor (JFET) p. 854
- 18-7 JFET Characteristics p. 856
- 18-8 The Metal-Oxide Semiconductor FET (MOSFET) p. 860
- 18-9 FET Biasing p. 863
- 18-10 Unijunction Transistors (UJTs) p. 867
- 18-11 Thyristors p. 869
- 18-12 Transistor Packages and Terminal Identification p. 871
- 18-13 Troubleshooting p. 874
- Application Assignment: Putting Your Knowledge to Work p. 879
- 19 Amplifiers and Oscillators p. 894
- 19-1 Common-Emitter Amplifiers p. 896
- 19-5 Multistage Amplifiers p. 914
- 19-2 Common-Collector Amplifiers p. 902
- 19-3 Common-Base Amplifiers p. 905
- 19-4 FET Amplifiers p. 908
- 19-6 Class A Operation p. 917
- 19-7 Class B Push-Pull Amplifier Operation p. 920
- 19-8 Class C Operation p. 926
- 19-9 Oscillators p. 930
- 19-10 Troubleshooting p. 936
- Application Assignment: Putting Your Knowledge to Work p. 940
- 20 Operational Amplifiers (Op-Amps) p. 954
- 20-1 Introduction to Operational Amplifiers p. 956
- 20-2 The Differential Amplifier p. 957
- 20-3 Op-Amp Parameters p. 965
- 20-4 Negative Feedback p. 971
- 20-5 Op-Amp Configurations with Negative Feedback p. 973
- 20-6 Op-Amp Impedances p. 978
- 20-7 Troubleshooting p. 981
- Application Assignment: Putting Your Knowledge to Work p. 984
- 21 Basic Applications of Op-Amps p. 996
- 21-1 Comparators p. 998
- 21-2 Summing Amplifiers p. 1001
- 21-3 Integrators and Differentiators p. 1006
- 21-4 Oscillators p. 1012
- 21-5 Active Filters p. 1022
- 21-6 Voltage Regulator Fundamentals p. 1030
- 21-7 Application Assignment: Putting Your Knowledge to Work p. 1036
- Appendices
- A Table of Standard Resistor Values p. 1
- B Batteries p. 2
- C Capacitor Color Coding and Marking p. 5
- D The Current Source, Norton's Theorem, and Millman's Theorem p. 9
- E Devices Data Sheets p. 15
- Answers to Odd-Numbered Problems p. 25
- Glossary p. 37

- Index p. 47