

Table of contents

- **1 Introduction to Operational Amplifiers**
- **2 Interpretation of Data Sheets and Characteristics of an Op-Amp**
- **3 An Op-Amp with Negative Feedback**
- **4 The Practical Op-Amp**
- **5 Frequency Response of an Op-Amp**
- **6 General Linear Applications**
- **7 Active Filters and Oscillators**
- **8 Comparators and Converters**
- **9 Specialized IC Applications**
- **10 Selected IC System Projects**
- **Appendix A Resistance Chart**
- **Appendix B Capacitance Chart**
- **Appendix C Important Derivations**
- **Appendix D Data Sheets**
- **Appendix E Answers to Selected Problems**
- **Bibliography**
- **Index**