

# Table of contents

- **1 Introduction**
- **2 Current and Voltage**
- **3 Resistance**
- **4 Ohm's Law, Power, and Energy**
- **5 Series Circuits**
- **6 Parallel Circuits**
- **7 Series-Parallel Networks**
- **8 Methods of Analysis and Selected Topics (dc)**
- **9 Network Theorems**
- **10 Capacitors**
- **11 Magnetic Circuits**
- **12 Inductors**
- **13 Sinusoidal Alternating Waveforms**
- **14 The Basic Elements and Phasors**
- **15 Series and Parallel ac Circuits**
- **16 Series-Parallel ac Networks**
- **17 Methods of Analysis and Selected Topics (ac)**
- **18 Network Theorems (ac)**
- **19 Power (ac)**
- **20 Resonance**
- **21 Decibels, Filters, and Bode Plots**
- **22 Pulse Waveforms and the R-C Response**
- **23 Polyphase Systems**
- **24 Nonsinusoidal Circuits**
- **25 Transformers**
- **26 System Analysis An Introduction**
- **Appendices**
- **Index**