

- Chapter 1 Introduction and Basic Concepts
 - 1 Role and Importance of Circuits in Engineering
 - 2 Fields, Charge, and Current
 - 3 Voltage
 - 4 Energy Conversion in an Electric Circuit
 - 5 Relationships among Voltage, Current, Power, and Energy
 - Power and Energy for Direct Voltages and Currents: Non-DC Power and Energy Calculations
 - 6 Ideal Voltage and Current Sources
 - 7 Resistance, Ohm's Law, and Power (a Reprise)
 - 8 Additional Concepts
 - Characteristics, Memoryless, Model, and Lumped V-I Characteristic of Constant Voltage and Current Sources
 - Notion of a Memoryless Device
 - Notion of Model
 - Frequency, Wavelength, and the Notion of a Lumped Circuit Element
 - Summary
 - Terms and Concepts
 - Problems
- Chapter 2 Kirchhoff's Current and Voltage Laws and Series-Parallel Resistive Circuits
 - 1 Introduction
 - 2 Terminology: Parallel, Series, Node, Branch, and so on
 - 3 Kirchhoff's Current Law
 - 4 Kirchhoff's Voltage Law
 - 5 Equivalent Resistance, Series Resistances, and Voltage Division
 - 6 Parallel Resistances and Current Division
 - 7 Series-Parallel Interconnections
 - 8 Dependent Sources Revisited
 - 9 Model for a Nonideal Battery and Battery Capacity
 - 10 Nonideal Sources
 - Summary
 - Problems
- Chapter 3 Nodal and Loop Analysis
 - I Introduction, Review, and Terminology
 - 2 Concepts of Nodal and Loop Analysis
 - 3 Nodal Analysis
 - I Grounded Voltage Sources
 - 4 Nodal Analysis
 - II Floating Voltage Sources
 - 5 Loop Analysis
 - 6 Modified Nodal Analysis
 - 7 Some Theoretical Foundations
 - Planar and Nonplanar Circuit Graphs
 - Meshes and Loops for Nonplanar Circuits
 - Number of Independent KCL and KVL Equations
- Chapter 4 The Operational Amplifier

- 1 Introduction
- 2 The Ideal Operational Amplifier
- 3 Design of General Summing Amplifiers
 - Design Choices for the General Summing Circuit
 - Derivation of Op Amp Input-Output Characteristic
- 4 Saturation and the Active Region of the Op Amp
- 5 Op Amp Circuit for Digital-to-Analog Conversion
 - Elements of A/D and D/A Conversion
 - Binary-Weighted Summing Circuit
 - Summary
 - Terms and Concepts
 - Problems
- Chapter 5 Linearity, Superposition, and Source Transformations
 - 1 Introduction
 - 2 Linearity
 - 3 Superposition and Proportionality
 - 4 Source Transformations
 - 5 Modified Superposition Analysis
 - Summary
 - Terms and Concepts
 - Problems
- Chapter 6 Thevenin, Norton, and Maximum Power Transfer Theorems
 - 1 Introduction
 - 2. Thevenin and Norton Equivalent Circuits for Passive Networks
 - 3 Thevenin and Norton Equivalent Circuits for Active Networks
 - 4 Thevenin and Norton Equivalent Circuits for Op Amp Circuits
 - 5 Thevenin and Norton Equivalent Circuits from Measured Data
 - 6 Theoretical Considerations: Pathological Cases and a Proof
 - 7 Maximum Power Transfer Theorem
 - Summary
 - Terms and Concepts
 - Problems
- Chapter 7 Inductors, Capacitors, and Duality
 - 1 Introduction
 - 2 The Inductor Some Physics: Definition and Basic Examples
 - 3 The Capacitor
 - Definitions and Properties
 - Relationship of Charge to Capacitor Voltage and Current
 - Principle of Conservation of Charge
 - Energy Storage in a Capacitor
 - Capacitance and Dielectrics
 - 4 Series and Parallel Inductors and Capacitors
 - Inductors in Series
 - Inductors in Parallel
 - Series-Parallel Inductor Combinations
 - Capacitors in Series
 - Capacitors in Parallel

- Series-Parallel Capacitor Combinations
- 5 Smoothing Property of a Capacitor in a Power Supply
- 6 The Duality Principle
- Basic Relationship of Dual Circuits
- Constructing the Dual N^* of a Planar Circuit N
- Summary
- Terms and Concepts
- Problems
- Chapter 8 First-Order RL and RC Circuits
- 1 Introduction
- 2 Some Mathematical Preliminaries
- 3 Source-Free or Zero-Input Response
- 4 DC or Step Response of First-Order Circuits
- 5 Superposition and Linearity
- 6 Response Classifications
- 7 Further Points of Analysis and Theory
- 8 First-Order RC Op Amp Circuits
- Summary
- Terms and Concepts
- Problems
- Chapter 9 Second-Order Linear Circuits
- 1 Introduction
- 2 Discharging a Capacitor through an Inductor
- 3 Source-Free Second-Order Linear Networks
- Development of Differential Equation Models for Series and Parallel RLC Circuits
- Solution of the Gene