

- Part 1 Introduction
- Chapter 1 Power Electronic Systems
- Chapter 2 Overview of Power Semiconductor Switches
- Chapter 3 Review of Basic Electrical and Magnetic Circuit Concepts
- Chapter 4 Computer Simulation of Power Electronic Converters and Systems
- Part 2 Generic Power Electronic Circuits
- Chapter 5 Line-Frequency Diode Rectifiers: Line-Frequency ac Uncontrolled dc
- Chapter 6 Line-Frequency Phase-Controlled Rectifiers and Inverters: Line-Frequency ac Controlled dc
- Chapter 7 dc-dc Switch-Mode Converters
- Chapter 8 Switch-Mode dc-ac Inverters: dc Sinusoidal ac
- Chapter 9 Resonant Converters: Zero-Voltage and/or Zero-Current Switchings
- Part 3 Power Supply Applications
- Chapter 10 Switching dc Power Supplies
- Chapter 11 Power Conditioners and Uninterruptible Power Supplies
- Part 4 Motor Drive Applications
- Chapter 12 Introduction to Motor Drives
- Chapter 13 dc Motor Drives
- Chapter 14 Induction Motor Drives
- Chapter 15 Synchronous Motor Drives
- Part 5 Other Applications
- Chapter 16 Residential and Industrial Applications
- Chapter 17 Electric Utility Applications
- Chapter 18 Optimizing the Utility Interface with Power Electronic Systems
- Part 6 Semiconductor Devices
- Chapter 19 Basic Semiconductor Physics
- Chapter 20 Power Diodes
- Chapter 21 Bipolar Junction Transistors
- Chapter 22 Power MOSFETs
- Chapter 23 Thyristors
- Chapter 24 Gate Turn-Off Thyristors
- Chapter 25 Insulated Gate Bipolar Transistors
- Chapter 26 Emerging Devices and Circuits
- Part 7 Practical Converter Design Considerations
- Chapter 27 Snubber Circuits
- Chapter 28 Gate and Base Drive Circuits
- Chapter 29 Component Temperature Control and Heat Sinks
- Chapter 30 Design of Magnetic Components
- Index