

Table of Contents

- Chapter 1 Models for Integrated-Circuit Active Devices p. 1
- 1.1 Introduction p. 1
- 1.2 Depletion Region of a pn Junction p. 1
- 1.3 Large-Signal Behavior of Bipolar Transistors p. 8
- 1.4 Small-Signal Models of Bipolar Transistors p. 26
- 1.5 Large Signal Behavior of Metal-Oxide-Semiconductor Field-Effect Transistors p. 38
- 1.6 Small-Signal Models of the MOS Transistors p. 49
- 1.7 Short-Channel Effects in MOS Transistors p. 58
- 1.8 Weak Inversion in MOS Transistors p. 65
- 1.9 Substrate Current Flow in MOS Transistors p. 71
- A.1.1 Summary of Active-Device Parameters p. 73
- Chapter 2 Bipolar, MOS, and BiCMOS Integrated-Circuit Technology p. 78
- 2.1 Introduction p. 78
- 2.2 Basic Processes in Integrated-Circuit Fabrication p. 79
- 2.3 High-Voltage Bipolar Integrated-Circuit Fabrication p. 88
- 2.4 Advanced Bipolar Integrated-Circuit Fabrication p. 92
- 2.5 Active Devices in Bipolar Analog Integrated Circuits p. 95
- 2.6 Passive Components in Bipolar Integrated Circuits p. 115
- 2.7 Modifications to the Basic Bipolar Process p. 123
- 2.8 MOS Integrated-Circuit Fabrication p. 127
- 2.9 Active Devices in MOS Integrated Circuits p. 131
- 2.10 Passive Components in MOS Technology p. 144
- 2.11 BiCMOS Technology p. 150
- 2.12 Heterojunction Bipolar Transistors p. 152
- 2.13 Interconnect Delay p. 153
- 2.14 Economics of Integrated-Circuit Fabrication p. 154
- 2.15 Packaging Considerations for Integrated Circuits p. 159
- A.2.1 SPICE Model-Parameter Files p. 163
- Chapter 3 Single-Transistor and Multiple-Transistor Amplifiers p. 170
- 3.1 Device Model Selection for Approximate Analysis of Analog Circuits p. 171
- 3.2 Two-Port Modeling of Amplifiers p. 172
- 3.3 Basic Single-Transistor Amplifier Stages p. 174
- 3.4 Multiple-Transistor Amplifier Stages p. 202
- 3.5 Differential Pairs p. 215
- A.3.1 Elementary Statistics and the Gaussian Distribution p. 246
- Chapter 4 Current Mirrors, Active Loads, and References p. 253
- 4.1 Introduction p. 253
- 4.2 Current Mirrors p. 253
- 4.3 Active Loads p. 278
- 4.4 Voltage and Current References p. 299
- A.4.1 Matching Considerations in Current Mirrors p. 327
- A.4.2 Input Offset Voltage of Differential Pair with Active Load p. 332
- Chapter 5 Output Stages p. 344
- 5.1 Introduction p. 344

- 6.1 Applications of Operational Amplifiers p. 405
- 5.2 The Emitter Follower As an Output Stage p. 344
- 5.3 The Source Follower As an Output Stage p. 356
- 5.4 Class B Push-Pull Output Stage p. 362
- 5.5 CMOS Class AB Output Stages p. 382
- Chapter 6 Operational Amplifiers with Single-Ended Outputs p. 404
- 6.2 Deviations from Ideality in Real Operational Amplifiers p. 419
- 6.3 Basic Two-Stage MOS Operational Amplifiers p. 425
- 6.4 Two-Stage MOS Operational Amplifiers with Cascodes p. 442
- 6.5 MOS Telescopic-Cascode Operational Amplifiers p. 444
- 6.6 MOS Folded-Cascode Operational Amplifiers p. 446
- 6.7 MOS Active-Cascode Operational Amplifiers p. 450
- 7.1 Introduction p. 488
- 6.8 Bipolar Operational Amplifiers p. 453
- 6.9 Design Considerations for Bipolar Monolithic Operational Amplifiers p. 472
- Chapter 7 Frequency Response of Integrated Circuits p. 488
- 7.2 Single-Stage Amplifiers p. 488
- 7.3 Multistage Amplifier Frequency Response p. 516
- 7.4 Analysis of the Frequency Response of the 741 Op Amp p. 537
- 7.5 Relation Between Frequency Response and Time Response p. 542
- Chapter 8 Feedback p. 553
- 8.1 Ideal Feedback Equation p. 553
- 8.2 Gain Sensitivity p. 555
- 8.3 Effect of Negative Feedback on Distortion p. 555
- 8.4 Feedback Configurations p. 557
- 8.5 Practical Configurations and the Effect of Loading p. 563
- 8.6 Single-Stage Feedback p. 587
- 8.7 The Voltage Regulator as a Feedback Circuit p. 593
- 8.8 Feedback Circuit Analysis Using Return Ratio p. 599
- 8.9 Modeling Input and Output Ports in Feedback Circuits p. 613
- Chapter 9 Frequency Response and Stability of Feedback Amplifiers p. 624
- 9.1 Introduction p. 624
- 9.2 Relation Between Gain and Bandwidth in Feedback Amplifiers p. 624
- 9.3 Instability and the Nyquist Criterion p. 626
- 9.4 Compensation p. 633
- 9.5 Root-Locus Techniques p. 664
- 9.6 Slew Rate p. 680
- A.9.1 Analysis in Terms of Return-Ratio Parameters p. 691
- A.9.2 Roots of a Quadratic Equation p. 692
- Chapter 10 Nonlinear Analog Circuits p. 702
- 10.1 Introduction p. 702
- 10.2 Precision Rectification p. 702
- 10.3 Analog Multipliers Employing the Bipolar Transistor p. 708
- 10.4 Phase-Locked Loops (PLL) p. 720
- 10.5 Nonlinear Function Symbols p. 743
- Chapter 11 Noise in Integrated Circuits p. 748

- 11.1 Introduction p. 748
- 11.2 Sources of Noise p. 748
- 11.3 Noise Models of Integrated-Circuit Components p. 756
- 11.4 Circuit Noise Calculations p. 760
- 11.5 Equivalent Input Noise Generators p. 768
- 11.6 Effect of Feedback on Noise Performance p. 776
- 11.7 Noise Performance of Other Transistor Configurations p. 783
- 11.8 Noise in Operational Amplifiers p. 788
- 11.9 Noise Bandwidth p. 794
- 11.10 Noise Figure and Noise Temperature p. 799
- Chapter 12 Fully Differential Operational Amplifiers p. 808
- 12.1 Introduction p. 808
- 12.2 Properties of Fully Differential Amplifiers p. 808
- 12.3 Small-Signal Models for Balanced Differential Amplifiers p. 811
- 12.4 Common-Mode Feedback p. 816
- 12.5 CMFB Circuits p. 823
- 12.6 Fully Differential Op Amps p. 835
- 12.7 Unbalanced Fully Differential Circuits p. 850
- 12.8 Bandwidth of the CMFB Loop p. 856
- Index p. 865