

- Preface
- 1 Introduction
- 2 Transfer functions
- 3 The extra element theorem
- 4 The N extra element theorem
- 5 Electronic negative feedback
- 6 High-frequency and microwave circuits
- 7 Passive filters
- 8 PWM switching DC-to-DC converters