

Table of contents

- **Preface** (p. ix)
- **1 Fundamentals**
- **1.1 Introduction** (p. 1)
- **1.2 The ideal op-amp** (p. 2)
- **1.3 Feedback and the ideal op-amp** (p. 2)
- **1.4 More examples of the ideal op-amp at work** (p. 4)
- **1.5 Op-amp packages** (p. 8)
- **Exercises** (p. 9)
- **2 Real op-amp performance parameters**
- **2.1 Op-amp input and output limitations** (p. 11)
- **2.2 Limitations in gain, and input and output impedance** (p. 13)
- **2.3 Real op-amp frequency response characteristics** (p. 19)
- **2.4 Small-signal closed-loop frequency response** (p. 22)
- **2.5 Closed-loop stability considerations** (p. 25)
- **2.6 Frequency compensation (phase compensation)** (p. 28)
- **2.7 Transient response characteristics** (p. 37)
- **2.8 Full power response** (p. 44)
- **2.9 Offsets, bias current and drift** (p. 45)
- **2.10 Common mode rejection ratio (CMRR)** (p. 49)
- **2.11 Noise in op-amp circuits** (p. 50)
- **Exercises** (p. 59)
- **3 Analogue integrated circuit technology**
- **3.1 Voltage feedback op-amps** (p. 64)
- **3.2 Comparison of voltage feedback op-amps** (p. 69)
- **3.3 Current feedback op-amps** (p. 72)
- **Exercises** (p. 81)
- **4 Applications: linear circuits**
- **4.1 Introduction** (p. 82)
- **4.2 Voltage scaling and buffer circuits** (p. 83)
- **4.3 Voltage summation** (p. 87)
- **4.4 Differential input amplifier configurations (voltage subtractor)** (p. 88)
- **4.5 Current scaling** (p. 93)
- **4.6 Voltage-to-current conversion** (p. 99)
- **4.7 AC amplifiers** (p. 104)
- **Exercises** (p. 105)
- **5 Logarithmic amplifiers and related circuits**
- **5.1 Amplifiers with defined non-linearity** (p. 107)
- **5.2 Synthesized non-linear response** (p. 108)
- **5.3 Logarithmic conversion with an inherently logarithmic device** (p. 111)
- **5.4 Logarithmic amplifiers: practical design considerations** (p. 119)
- **5.5 Some practical log and antilog circuit configurations** (p. 129)
- **5.6 Log and antilog circuits for computation** (p. 137)
- **5.7 A variable transconductance four quadrant multiplier** (p. 139)
- **Exercises** (p. 142)

- **6 Integrators and differentiators**
- **6.1 The basic integrator** (p. 144)
- **6.2 Integrator run, set and hold modes** (p. 145)
- **6.3 Integrator errors** (p. 146)
- **6.4 Extensions to a basic integrator** (p. 153)
- **6.5 Integrator reset** (p. 158)
- **6.6 AC integrators** (p. 160)
- **6.7 Differentiators** (p. 161)
- **6.8 Practical considerations in differentiator design** (p. 163)
- **6.9 Modifications to the basic differentiator** (p. 166)
- **Exercises** (p. 166)
- **7 Comparator, monostable and oscillator circuits**
- **7.1 Comparators** (p. 169)
- **7.2 Multivibrators** (p. 173)
- **7.3 Sine wave oscillators** (p. 181)
- **7.4 Waveform generators** (p. 185)
- **7.5 The 555 timer** (p. 190)
- **7.6 The 8038 waveform generator** (p. 192)
- **Exercises** (p. 196)
- **8 Sensor interface, analogue processing and digital conversion**
- **8.1 Sensor interface circuits** (p. 197)
- **8.2 Hot wire anemometer with constant temperature operation** (p. 203)
- **8.3 Temperature measurement using a thermocouple** (p. 204)
- **8.4 Light sensitive switching** (p. 205)
- **8.5 Sensing analogue light levels** (p. 206)
- **8.6 Interfacing linear Hall effect transducers (LHETS)** (p. 206)
- **8.7 Precise diode circuits** (p. 207)
- **8.8 Full-wave rectifier circuits** (p. 209)
- **8.9 Peak detectors** (p. 211)
- **8.10 Sample and hold circuits** (p. 213)
- **8.11 Voltage-to-frequency conversion** (p. 215)
- **8.12 Frequency-to-voltage conversion** (p. 217)
- **8.13 Analogue-to-digital converter (ADC)** (p. 218)
- **8.14 Digital-to-analogue converter (DAC)** (p. 221)
- **Exercises** (p. 226)
- **9 Active filters**
- **9.1 Introduction** (p. 227)
- **9.2 Passive filters** (p. 227)
- **9.3 Active filters** (p. 237)
- **9.4 Active filters using operational amplifiers (op-amps)** (p. 238)
- **9.5 Choosing the frequency response of the low-pass filter** (p. 238)
- **9.6 Choosing the frequency response of the high-pass filter** (p. 243)
- **9.7 Band-pass filters using the state variable technique** (p. 245)
- **9.8 Band reject (notch filter)** (p. 248)
- **9.9 Phase shifting circuit (all-pass filter)** (p. 249)
- **9.10 Filter design** (p. 250)

- Exercises (p. 256)
- **10 Practical considerations**
- **10.1 Op-amp selection and design specification** (p. 257)
- **10.2 Selection processes** (p. 258)
- **10.3 Attention to external circuit details** (p. 260)
- **10.4 Avoiding unwanted signals** (p. 261)
- **10.5 Ensure closed-loop stability** (p. 265)
- **10.6 Offset nulling techniques** (p. 267)
- **10.7 Importance of external passive components** (p. 270)
- **10.8 Avoiding fault conditions** (p. 272)
- **10.9 Modifying an op-amp's output capability** (p. 273)
- **10.10 Speeding up a low drift op-amp** (p. 279)
- **10.11 Single power supply operation for op-amps** (p. 280)
- **10.12 Voltage regulator circuits** (p. 282)
- Exercises (p. 287)
- Bibliography (p. 289)
- Answers to exercises (p. 290)
- **Appendix A1 Operational amplifier applications and circuit ideas** (p. 294)
- **Appendix A2 Gain peaking/damping factor/phase margin** (p. 306)
- **Appendix A3 Effect of resistor tolerance on CMRR of one amplifier differential circuit** (p. 310)
- **Appendix A4 Instrumentation transducers** (p. 313)
- **A4.1 Introduction** (p. 313)
- **A4.2 Resistance strain gauges** (p. 313)
- **A4.3 Platinum resistance temperature detectors** (p. 315)
- **A4.4 Thermistors** (p. 317)
- **A4.5 Pressure transducers** (p. 317)
- **A4.6 Thermocouples** (p. 318)
- **A4.7 Linear variable differential transformer (LVDT)** (p. 319)
- **A4.8 Capacitive transducers** (p. 319)
- **A4.9 Tachometers** (p. 319)
- **A4.10 Electromagnetic flowmeters** (p. 320)
- **A4.11 Hall effect transducers** (p. 320)
- **A4.12 Opto transducers** (p. 321)
- **Appendix A5 Semiconductor data sheets** (p. 323)
- Index (p. 385)