

- Preface p. ix
- 1 Advanced Operational Amplifier Principles p. 1
  - Introduction p. 1
  - Objectives p. 1
  - 1.1 Op Amp Characteristics p. 2
    - Voltage Follower p. 5
    - Noninverting Amplifier p. 8
    - Inverting Amplifier p. 14
  - 1.2 A Universal Analysis Technique p. 20
    - Difference Amplifier p. 21
    - Instrumentation Amplifier p. 27
  - 1.3 Composite Amplifier p. 30
    - Power Output Stage p. 30
    - Active Feedback p. 33
  - 1.4 Suspended Supply Amplifier p. 35
    - Suspending the Supply p. 39
    - The Amplifier p. 43
    - Tolerances, Tolerances, Tolerances! p. 46
    - Composite Amplifier p. 49
    - Summary p. 52
    - Problems p. 54
    - Suspended Supply Amp Lab Exercise p. 59
- 2 Power Electronics Circuit Layout
  - Introduction p. 65
  - Objectives p. 65
  - 2.1 Mechanical and Thermal Details p. 66
  - 2.2 Part Placement p. 75
  - 2.3 Interconnections p. 83
    - Wire Gage p. 83
    - Traces p. 88
  - 2.4 Other Considerations p. 96
    - Summary p. 98
    - Problems p. 100
- 3 Power Parameter Calculations
  - Introduction p. 103
  - Objectives p. 103
  - 3.1 Common Waveforms p. 104
    - DC p. 104
    - Sinusoid p. 104
    - Rectangular Waves p. 107
    - Triangular Waves p. 108
  - 3.2 Average Value p. 111
    - Rectangular Waves p. 111
    - Sinusoids p. 113

- Triangular Waves p. 117
- 3.3 Root Mean Squared Value p. 122
- DC Value p. 123
- Rectangular Waves p. 123
- Triangular Waves p. 125
- Sinusoids p. 131
- 3.4 Power p. 136
- DC Voltage and Current p. 141
- Sinusoids p. 142
- Rectangular Waves p. 150
- Summary p. 152
- Problems p. 155
- 4 Linear Power Amplifier Integrated Circuits
- Introduction p. 159
- Objectives p. 159
- 4.1 OPA548 Operational Amplifier IC p. 160
- 4.2 Power Calculations p. 166
- DC Signal to the Load p. 166
- Sinusoidal Signal to the Load p. 171
- 4.3 Heat Sinks p. 176
- 4.4 Protecting the OPA548 p. 181
- 4.5 Audio Power Parameters p. 183
- 4.6 Low Power Audio Amplifier IC p. 189
- 4.7 High Power Audio Amplifier IC p. 198
- Summary p. 202
- Problems p. 204
- Power Op Amp Lab Exercise p. 208
- 5 Discrete Linear Power Amplifier
- Introduction p. 213
- Objectives p. 213
- 5.1 The Enhancement Mode MOSFET p. 214
- N-Channel p. 214
- P-Channel p. 218
- 5.2 Class A Common Drain Amplifier p. 220
- Bias p. 220
- AC Operation p. 221
- 5.3 Class B Push-Pull Amplifier p. 224
- The Push Amplifier p. 225
- The Pull Amplifier p. 229
- The Push-Pull Amplifier p. 230
- 5.4 Class B Amp with Op Amp Driver p. 233
- Noninverting Amplifier p. 233
- The Suspended Supply Amplifier p. 236
- Layout Concerns p. 237

- Inverting Amplifier p. 237
- Op Amp Selection p. 243
- 5.5 Parallel MOSFETs in a Linear Amp p. 245
- 5.6 Amplifier Protection p. 250
- Current Limiting p. 251
- Thermal Shutdown p. 254
- 5.7 Driving a Reactive Load p. 256
- Summary p. 259
- Problems p. 261
- Class B Amplifier Lab Exercise p. 263
- 6 Power Switches
- Introduction p. 269
- Objectives p. 269
- 6.1 Switching Characteristics p. 270
- Diodes p. 270
- Transistors p. 273
- 6.2 Parallel MOSFET Switches p. 280
- 6.3 Low Side Switches p. 281
- Bipolar Junction Transistor p. 281
- Open Collector Inverter p. 286
- MOSFET Low Side Switch p. 288
- 6.4 High Side Switches p. 295
- N-Channel High Side Switch p. 295
- P-Channel High Side Switch p. 296
- PNP High Side Switch p. 302
- 6.5 MOSFET Switch Drivers p. 304
- Low Side MOSFET Driver p. 305
- High and Low Side MOSFET Driver p. 307
- 6.6 H Bridge p. 309
- Summary p. 315
- Problems p. 316
- Transistor Switch Lab Exercise p. 321
- 7 Switching Power Supplies
- Introduction p. 325
- Objectives p. 325
- 7.1 Buck Regulators p. 326
- Basics p. 326
- LM2595 Simple Switcher Buck Regulator IC p. 337
- 7.2 Boost Regulators p. 344
- Basics p. 344
- LM2585 Simple Switcher Flyback Regulator IC p. 352
- 7.3 Line Voltage Flyback Converter p. 357
- The Flyback Converter p. 357
- Line Voltage Input p. 366

- Summary p. 372
- Problems p. 374
- Buck Regulator Lab Exercise p. 379
- Boost Regulator Lab Exercise p. 381
- 8 Thyristors
  - Introduction p. 385
  - Objectives p. 385
  - 8.1 Thyristor Device Characteristics p. 386
    - Silicon Controlled Rectifier p. 386
    - Triac p. 393
    - Low Side versus High Side Switch p. 395
  - 8.2 Snubbing p. 396
    - Critical Rate of Rise of Current p. 396
    - Critical Rate of Rise of Voltage p. 398
  - 8.3 Triggers p. 403
    - Shockley Diode p. 403
    - Diac p. 404
    - Optically Coupled Triac Trigger p. 406
  - 8.4 Proportional Power Circuits p. 409
    - Time Proportioning p. 410
    - Phase Angle Firing p. 417
  - Summary p. 431
  - Problems p. 433
  - Triac Lab Exercise p. 437
- 9 Power Conversion and Motor Drive Applications
  - Introduction p. 445
  - Objectives p. 445
  - 9.1 DC-to-DC Converters p. 446
    - Buck p. 446
    - Boost p. 450
    - Flyback Converter p. 453
  - 9.2 AC-to-DC Converters p. 455
    - Single-Phase p. 455
    - Three-Phase p. 464
  - 9.3 DC-to-AC Converters p. 477
    - Input Inverter p. 479
    - Secondaries p. 482
    - Microcontroller p. 482
    - H Bridge and Driver p. 486
    - Output Filter p. 488
    - Negative Feedback p. 490
  - 9.4 Permanent Magnet Motor Drivers p. 493
    - Common Concerns p. 493
    - DC Brush Motor p. 498

- DC Brushless Motor p. 502
- Summary p. 507
- Problems p. 509
- Appendix A Answers to Odd-Numbered Problems p. 513
- Appendix B Laboratory Parts and Special Equipment p. 517
- Index p. 519