

- Foreword p. xi
- Preface p. xiii
- 1 Introduction p. 1
- 1.1 Applications of RF and microwave filters p. 1
- 1.2 Ideal lowpass filters p. 5
- 1.3 Minimum phase networks p. 7
- 1.4 Amplitude approximation p. 10
- 1.5 Practical realisations of microwave filters p. 12
- 1.6 Summary p. 12
- 1.7 References p. 13
- 2 Basic network theory p. 15
- 2.1 Linear passive time-invariant networks p. 15
- 2.1.1 Linearity p. 16
- 2.1.2 Time invariance p. 16
- 2.1.3 Passivity p. 17
- 2.1.4 The bounded real condition p. 17
- 2.2 Lossless networks p. 18
- 2.3 Ladder networks p. 21
- 2.4 Synthesis of two-port networks--Darlington synthesis p. 22
- 2.4.1 Cascade synthesis p. 25
- 2.4.2 All-pole networks p. 29
- 2.5 Analysis of two-port networks--the ABCD matrix p. 29
- 2.6 Analysis of two-port networks--the scattering matrix p. 34
- 2.6.1 Relationships between ABCD parameters and S parameters p. 40
- 2.7 Even- and odd-mode analysis of symmetrical networks p. 41
- 2.8 Analysis by image parameters p. 44
- 2.9 Analysis of distributed circuits p. 46
- 2.10 Summary p. 47
- 2.11 References p. 48
- 3 Designs of lumped lowpass prototype networks p. 49
- 3.1 Introduction p. 49
- 3.2 The maximally flat prototype p. 49
- 3.2.1 Impedance inverters p. 55
- 3.3 The Chebyshev prototype p. 56
- 3.4 The elliptic function prototype p. 64
- 3.5 The generalised Chebyshev prototype p. 68
- 3.6 Filters with specified phase and group delay characteristics p. 71
- 3.6.1 The maximally flat group delay lowpass prototype p. 73
- 3.6.2 The equidistant linear phase approximation p. 75
- 3.6.3 Combined phase and amplitude approximation p. 77
- 3.7 Filters with specified time domain characteristics p. 78
- 3.8 Synthesis of generalised Chebyshev filters p. 81
- 3.8.1 Synthesis of generalised Chebyshev prototypes with symmetrically located transmission zeros p. 81

- 3.8.2 Synthesis of generalised Chebyshev prototypes with ladder-type networks p. 86
- 3.8.3 Asymmetrically located transmission zeros p. 90
- 3.9 Summary p. 98
- 3.10 References p. 99
- 4 Circuit transformations on lumped prototype networks p. 101
- 4.1 Introduction p. 101
- 4.2 Impedance transformations p. 101
- 4.2.1 Example p. 103
- 4.3 Lowpass to arbitrary cut-off frequency lowpass transformation p. 103
- 4.3.1 Example p. 104
- 4.4 Lowpass to highpass transformation p. 105
- 4.4.1 Example p. 106
- 4.5 Lowpass to bandpass transformation p. 107
- 4.5.1 Example p. 114
- 4.5.2 Nodal admittance matrix scaling p. 116
- 4.6 Lowpass to bandstop transformation p. 118
- 4.6.1 Design example p. 121
- 4.7 Effects of losses on bandpass filters p. 125
- 4.8 Practical procedures p. 131
- 4.8.1 Measurement of input coupling p. 131
- 4.8.2 Measurement of inter-resonator coupling p. 133
- 4.8.3 Measurement of resonator Q factor p. 134
- 4.9 Summary p. 135
- 4.10 References p. 136
- 5 TEM transmission line filters p. 137
- 5.1 Commensurate distributed circuits p. 137
- 5.2 Stepped impedance unit element prototypes p. 144
- 5.2.1 Physical realisation of stepped impedance lowpass filters p. 149
- 5.3 Broadband TEM filters with generalised Chebyshev characteristics p. 151
- 5.3.1 Generalised Chebyshev highpass filters p. 162
- 5.4 Parallel coupled transmission lines p. 165
- 5.5 The interdigital filter p. 167
- 5.5.1 Design example p. 173
- 5.5.2 Narrowband interdigital filters p. 174
- 5.5.3 Design example p. 176
- 5.5.4 Physical design of the interdigital filter p. 177
- 5.6 The combline filter p. 182
- 5.6.1 Design example p. 192
- 5.6.2 Tunable combline filters p. 194
- 5.7 The parallel coupled-line filter p. 194
- 5.8 Narrowband coaxial resonator filters p. 197
- 5.9 Summary p. 198
- 5.10 References p. 199
- 6 Waveguide filters p. 201

- 6.1 Introduction p. 201
- 6.2 Basic theory of waveguides p. 202
 - 6.2.1 TE modes p. 203
 - 6.2.2 TM modes p. 208
 - 6.2.3 Relative cut-off frequencies of modes p. 209
 - 6.2.4 Rectangular waveguide resonators p. 209
 - 6.2.5 Numerical example p. 210
 - 6.2.6 Spurious resonances p. 212
 - 6.2.7 Circular waveguides p. 212
 - 6.2.8 TE modes p. 213
 - 6.2.9 TM modes p. 215
 - 6.2.10 Circular waveguide resonators p. 217
 - 6.2.11 Numerical example p. 217
- 6.3 Design of waveguide bandpass filters p. 220
 - 6.3.1 Design example p. 228
- 6.4 The generalised direct-coupled cavity waveguide filter p. 230
- 6.5 Extracted pole waveguide filters p. 239
 - 6.5.1 Realisation in waveguide p. 249
 - 6.5.2 Design example p. 252
 - 6.5.3 Realisation in TE₀₁₁ mode cavities p. 254
- 6.6 Dual-mode waveguide filters p. 255
 - 6.6.1 Numerical example p. 263
 - 6.6.2 Asymmetric realisations for dual-mode filters p. 265
- 6.7 Summary p. 267
- 6.8 References p. 268
- 7 Dielectric resonator filters p. 271
 - 7.1 Introduction p. 271
 - 7.2 Dielectric rod waveguides and the TE_{01 Δ} mode p. 272
 - 7.3 Dual-mode dielectric resonator filters p. 283
 - 7.3.1 Dual-mode conductor-loaded dielectric resonator filters p. 285
 - 7.4 Triple-mode dielectric resonator filters p. 290
 - 7.4.1 Spherical dielectric resonators p. 290
 - 7.4.2 Cubic dielectric resonators p. 298
 - 7.4.3 Design of triple-mode dielectric resonator reflection filters p. 301
 - 7.4.4 Design example p. 305
 - 7.5 Dielectric-loaded filters p. 309
 - 7.5.1 Dielectric-loaded waveguide filters p. 314
 - 7.6 Summary p. 317
 - 7.7 References p. 318
- 8 Miniaturisation techniques for microwave filters p. 321
 - 8.1 Introduction p. 321
 - 8.2 Dielectric resonator filters p. 322
 - 8.3 Superconducting filters p. 322
 - 8.4 Surface acoustic wave filters p. 323

- 8.5 Active microwave filters p. 325
- 8.6 Lossy filters p. 327
- 8.6.1 Design of lossy filters--classical predistortion p. 331
- 8.6.2 Design of lossy filters--reflection mode type p. 335
- 8.6.3 Design example p. 339
- 8.7 Summary p. 343
- 8.8 References p. 344
- Index p. 345