Table of contents

- Characterization and Analysis of Linear Circuits at RF and Microwave Frequencies
- Characterization and Analysis of Active Circuits at RF and Microwave Frequencies
- Radio-Frequency Components
- Narrowband Impedance-Matching with LC Networks
- Coupled Coils and Transformers
- Transmission-Line Transformers
- Film Resistors and Single-Layer Parallel-Plate Capacitors
- The Design of Wide-Band Impedance-Matching Networks
- Microwave Lumped Elements, Distributed Equivalents, and Microstrip Parasitics
- The Design of Radio-Frequency and Microwave Amplifiers and Oscillators