

- Preface p. xv
- Chapter 1 Introductory Concepts and Fundamentals p. 1
  - Chapter Objectives p. 1
  - 1.1 Introduction p. 1
    - Variable Naming Convention p. 2
  - 1.2 The Decibel p. 3
    - Decibel Representation of Power and Voltage Gains p. 3
    - Signal Representation in dBW and dBV p. 8
    - Items of Interest in the Laboratory p. 11
  - 1.3 Bode Plots p. 12
    - Lead Network Gain Response p. 12
    - Lead Network Phase Response p. 15
    - Lag Network Response p. 17
    - Risetime Versus Bandwidth p. 20
  - 1.4 Combining the Elements--Multistage Effects p. 22
  - 1.5 Circuit Simulations Using Computers p. 24
  - 1.6 The Differential Amplifier p. 26
    - DC Analysis p. 27
    - Input Offset Current and Voltage p. 29
    - AC Analysis p. 30
    - Common Mode Rejection p. 36
    - Current Mirror p. 38
    - Summary p. 40
    - Review Questions p. 41
    - Problems p. 41
- Chapter 2 Operational Amplifier Internals p. 44
  - Chapter Objectives p. 44
  - 2.1 Introduction p. 44
  - 2.2 What Is an Op Amp? p. 45
    - Block Diagram of an Op Amp p. 46
    - A Simple Op Amp Simulation Model p. 50
    - Op Amp Data Sheet and Interpretation p. 52
    - Simple Op Amp Comparator p. 55
  - 2.3 Op Amp Manufacture p. 60
    - Monolithic Construction p. 61
    - Hybrid Construction p. 63
    - Summary p. 63
    - Review Questions p. 63
    - Problems p. 64
- Chapter 3 Negative Feedback p. 66
  - Chapter Objectives p. 66
  - 3.1 Introduction p. 66
  - 3.2 What Negative Feedback Is and Why We Use It p. 67
  - 3.3 Basic Concepts p. 67
    - The Effects of Negative Feedback p. 68
  - 3.4 The Four Variants of Negative Feedback p. 70

- Series-Parallel (SP) p. 72
- SP Impedance Effects p. 79
- Distortion Effects p. 84
- Noise p. 88
- Parallel-Series (PS) p. 89
- PS Impedance Effects p. 93
- Parallel-Parallel (PP) and Series-Series (SS) p. 95
- 3.5 Limitations on the Use of Negative Feedback p. 96
- Summary p. 97
- Review Questions p. 97
- Problems p. 97
- Chapter 4 Basic Op Amp Circuits p. 100
- Chapter Objectives p. 100
- 4.1 Introduction p. 100
- 4.2 Inverting and Noninverting Amplifiers p. 101
- The Noninverting Voltage Amplifier p. 101
- Inverting Voltage Amplifier p. 105
- Inverting Current-to-Voltage Transducer p. 110
- Noninverting Voltage-to-Current Transducer p. 111
- Inverting Current Amplifier p. 114
- Summing Amplifiers p. 117
- Noninverting Summing Amplifier p. 120
- Differential Amplifier p. 123
- Adder/Subtractor p. 125
- Adjustable Inverter/Noninverter p. 126
- 4.3 Single-Supply Biasing p. 128
- 4.4 Current Boosting p. 131
- Summary p. 132
- Review Questions p. 133
- Problems p. 134
- Chapter 5 Practical Limitations of Op Amp Circuits p. 138
- Chapter Objectives p. 138
- 5.1 Introduction p. 138
- 5.2 Frequency Response p. 139
- 5.3 Gain-Bandwidth Product p. 139
- Multistage Considerations p. 146
- Low-Frequency Limitations p. 150
- 5.4 Slew Rate and Power Bandwidth p. 152
- The Effect of Slew Rate on Pulse Signals p. 153
- The Effect of Slew Rate on Sinusoidal Signals and Power Bandwidth p. 153
- Design Hint p. 157
- Slew Rate and Multiple Stages p. 158
- Noncompensated Devices p. 161
- Feedforward Compensation p. 162
- Decompensated Devices p. 163
- 5.5 Offsets p. 164

- Offset Sources and Compensation p. 164
- 5.6 Drift p. 170
- 5.7 CMRR and PSRR p. 173
- 5.8 Noise p. 175
- Summary p. 180
- Review Questions p. 181
- Problems p. 181
- Chapter 6 Specialized Op Amps p. 183
- Chapter Objectives p. 183
- 6.1 Introduction p. 183
- 6.2 Instrumentation Amplifiers p. 184
- 6.3 Programmable Op Amps p. 193
- 6.4 Op Amps for High Current, Power, and Voltage Applications p. 197
- High-Current Devices p. 197
- High-Voltage Devices p. 201
- 6.5 High-Speed Amplifiers p. 201
- 6.6 Voltage Followers and Buffers p. 202
- 6.7 Operational Transconductance Amplifier p. 204
- 6.8 Norton Amplifier p. 207
- 6.9 Current Feedback Amplifiers p. 214
- 6.10 Other Specialized Devices p. 217
- Summary p. 220
- Review Questions p. 220
- Problems p. 221
- Chapter 7 Nonlinear Circuits p. 223
- Chapter Objectives p. 223
- 7.1 Introduction p. 223
- 7.2 Precision Rectifiers p. 224
- Peak Detector p. 227
- Precision Full-Wave Rectifier p. 232
- 7.3 Wave Shaping p. 235
- Active Clampers p. 235
- Active Limiters p. 240
- 7.4 Function Generation p. 244
- 7.5 Comparators p. 254
- 7.6 Log and Anti-Log Amplifiers p. 266
- Four-Quadrant Multiplier p. 270
- 7.7 Extended Topic: A Precision Log Amp p. 273
- Summary p. 276
- Review Questions p. 277
- Problems p. 277
- Chapter 8 Voltage Regulation p. 280
- Chapter Objectives p. 280
- 8.1 Introduction p. 280
- 8.2 The Need for Regulation p. 281
- 8.3 Linear Regulators p. 283

- Three Terminal Devices p. 287
- Current Boosting p. 292
- Low Dropout Regulators p. 292
- Programmable and Tracking Regulators p. 293
- 8.4 Switching Regulators p. 307
- 8.5 Heat Sink Usage p. 317
- Physical Requirements p. 317
- Thermal Resistance p. 317
- 8.6 Extended Topic: Primary Switcher p. 322
- Summary p. 323
- Review Questions p. 324
- Problems p. 324
- Chapter 9 Oscillators and Frequency Generators p. 326
- Chapter Objectives p. 326
- 9.1 Introduction p. 326
- 9.2 Op Amp Oscillators p. 327
- Positive Feedback and the Barkhausen Criterion p. 327
- A Basic Oscillator p. 328
- Wien Bridge Oscillator p. 329
- Phase Shift Oscillator p. 335
- Square/Triangle Function Generator p. 343
- 9.3 Single-Chip Oscillators and Frequency Generators p. 354
- Voltage-Controlled Oscillator p. 354
- Phase-Locked Loop p. 359
- 555 Timer p. 364
- 555 Monostable Operation p. 365
- 555 Astable Operation p. 367
- Waveform Generator p. 370
- Summary p. 376
- Review Questions p. 376
- Problems p. 377
- Chapter 10 Integrators and Differentiators p. 380
- Chapter Objectives p. 380
- 10.1 Introduction p. 380
- 10.2 Integrators p. 381
- Accuracy and Usefulness of Integration p. 383
- Optimizing the Integrator p. 383
- Analyzing Integrators with the Time-Continuous Method p. 387
- Analyzing Integrators with the Time-Discrete Method p. 388
- 10.3 Differentiators p. 393
- Accuracy and Usefulness of Differentiation p. 394
- Optimizing the Differentiator p. 395
- Analyzing Differentiators with the Time-Continuous Method p. 397
- Analyzing Differentiators with the Time-Discrete Method p. 398
- 10.4 Analog Computer p. 407
- 10.5 Alternatives to Integrators and Differentiators p. 409

- 10.6 Extended Topic: Other Integrator and Differentiator Circuits p. 410
- Summary p. 412
- Review Questions p. 412
- Problems p. 413
- Chapter 11 Active Filters p. 416
- Chapter Objectives p. 416
- 11.1 Introduction p. 416
- 11.2 Filter Types p. 417
- 11.3 The Use and Advantages of Active Filters p. 419
- 11.4 Filter Order and Poles p. 420
- 11.5 Filter Class or Alignment p. 422
- Butterworth p. 423
- Bessel p. 423
- Chebyshev p. 424
- Elliptic p. 425
- Other Possibilities p. 426
- 11.6 Realizing Practical Filters p. 426
- Sallen and Key VCVS Filters p. 426
- Sallen and Key Low-Pass Filters p. 428
- Sallen and Key High-Pass Filters p. 439
- Filters of Higher Order p. 442
- 11.7 Band-Pass Filter Realizations p. 452
- Multiple-Feedback Filters p. 454
- State-Variable Filter p. 459
- 11.8 Notch Filter (Band-Reject) Realizations p. 465
- A Note on Component Selection p. 467
- Filter Design Tools p. 468
- 11.9 Audio Equalizers p. 469
- 11.10 Switched-Capacitor Filters p. 474
- 11.11 Extended Topic: Voltage-Controlled Filters p. 479
- Summary p. 481
- Review Questions p. 482
- Problems p. 482
- Chapter 12 Analog-to-Digital-to-Analog Conversion p. 484
- Chapter Objectives p. 484
- 12.1 Introduction p. 484
- The Advantages and Disadvantages of Working in the Digital Domain p. 485
- 12.2 The Sampling Theorem p. 486
- 12.3 Resolution and Sampling Rate p. 488
- 12.4 Digital-to-Analog Conversion Techniques p. 492
- Practical Digital-to-Analog Converter Limits p. 496
- Digital-to-Analog Converter Integrated Circuits p. 501
- Applications of Digital-to-Analog Converter Integrated Circuits p. 506
- 12.5 Analog-to-Digital Conversion p. 512
- Analog-to-Digital Conversion Techniques p. 515
- Analog-to-Digital Converter Integrated Circuits p. 520

- Applications of Analog-to-Digital Converter Integrated Circuits p. 526
- 12.6 Extended Topic: Digital Signal Processing p. 529
- Summary p. 532
- Review Questions p. 533
- Problems p. 533
- Appendix A Data Sheets p. 535
- Appendix B Answers to Odd-Numbered Review Questions p. 536
- Appendix C Answers to Odd-Numbered Problem Sets p. 542
- Index p. 589