

- Acknowledgments p. ix
- Chapter 1 Introduction p. 1
- 1.1 Motivation p. 1
- 1.2 Historical Perspective p. 2
- 1.3 Linearization and Memory Effects p. 3
- 1.4 Main Contents of the Book p. 4
- 1.5 Outline of the Book p. 6
- References p. 8
- Chapter 2 Some Circuit Theory and Terminology p. 9
- 2.1 Classification of Electrical Systems p. 10
- 2.1.1 Linear Systems and Memory p. 10
- 2.1.2 Nonlinear Systems p. 13
- 2.1.3 Common Measures of Nonlinearity p. 15
- 2.2 Calculating Spectrums in Nonlinear Systems p. 18
- 2.3 Memoryless Spectral Regrowth p. 21
- 2.4 Signal Bandwidth Dependent Nonlinear Effects p. 25
- 2.5 Analysis of Nonlinear Systems p. 27
- 2.5.1 Volterra Series Analysis p. 28
- 2.5.2 Direct Calculation of Nonlinear Responses p. 30
- 2.5.3 Two Volterra Modeling Approaches p. 34
- 2.6 Summary p. 39
- 2.7 Key Points to Remember p. 41
- References p. 41
- Chapter 3 Memory Effects in RF Power Amplifiers p. 43
- 3.1 Efficiency p. 43
- 3.2 Linearization p. 45
- 3.2.1 Linearization and Efficiency p. 45
- 3.2.2 Linearization Techniques p. 46
- 3.2.3 Linearization and Memory Effects p. 48
- 3.3 Electrical Memory Effects p. 51
- 3.4 Electrothermal Memory Effects p. 56
- 3.5 Amplitude Domain Effects p. 59
- 3.5.1 Fifth-Order Analysis Without Memory Effects p. 60
- 3.5.2 Fifth-Order Analysis with Memory Effects p. 62
- 3.6 Summary p. 66
- 3.7 Key Points to Remember p. 67
- References p. 68
- Chapter 4 The Volterra Model p. 71
- 4.1 Nonlinear Modeling p. 71
- 4.1.1 Nonlinear Simulation Models p. 72
- 4.1.2 The Properties of the Volterra Models p. 75
- 4.2 Nonlinear I-V and Q-V Characteristics p. 77
- 4.2.1 $I_{[C]}-V_{[BE]}-V_{[CE]}$ Characteristic p. 78
- 4.2.2 $g_{[\pi]}$ and $r_{[bb]}$ p. 82
- 4.2.3 Capacitance Models p. 82
- 4.3 Model of a Common-Emitter BJT/HBT Amplifier p. 84

- 4.3.1 Linear Analysis p. 84
- 4.3.2 Nonlinear Analysis p. 87
- 4.4 IM3 in a BJT CE Amplifier p. 95
- 4.4.1 BJT as a Cascade of Two Nonlinear Blocks p. 95
- 4.4.2 Detailed BJT Analysis p. 102
- 4.5 MESFET Model and Analysis p. 109
- 4.6 Summary p. 115
- 4.7 Key Points to Remember p. 117
- References p. 118
- Chapter 5 Characterization of Volterra Models p. 123
- 5.1 Fitting Polynomial Models p. 124
- 5.1.1 Exact and LMSE Fitting p. 124
- 5.1.2 Effects of Fitting Range p. 126
- 5.2 Self-Heating Effects p. 127
- 5.2.1 Pulsed Measurements p. 129
- 5.2.2 Thermal Operating Point p. 131
- 5.3 DC I-V Characterization p. 133
- 5.3.1 Pulsed DC Measurement Setup p. 133
- 5.5.1 Test Setup p. 137
- 5.3.2 Fitting I-V Measurements p. 134
- 5.4 AC Characterization Flow p. 136
- 5.5 Pulsed S-Parameter Measurements p. 137
- 5.5.2 Calibration p. 139
- 5.6 De-embedding the Effects of the Package p. 140
- 5.6.1 Full 4-Port De-embedding p. 141
- 5.6.2 De-embedding Plain Bonding Wires p. 143
- 5.7 Calculation of Small-Signal Parameters p. 145
- 5.8 Fitting the AC Measurements p. 147
- 5.8.1 Fitting of Nonlinear Capacitances p. 147
- 5.8.2 Fitting of Drain Current Nonlinearities p. 149
- 5.9 Nonlinear Model of a 1-W BJT p. 152
- 5.10 Nonlinear Model of a 1-W MESFET p. 155
- 5.11 Nonlinear Model of a 30-W LDMOS p. 160
- 5.12 Summary p. 165
- 5.13 Key Points to Remember p. 166
- References p. 167
- Chapter 6 Simulating and Measuring Memory Effects p. 171
- 6.1 Simulating Memory Effects p. 172
- 6.1.1 Normalization of IM3 Components p. 172
- 6.1.2 Simulation of Normalized IM3 Components p. 175
- 6.2 Measuring the Memory Effects p. 180
- 6.2.1 Test Setup and Calibration p. 181
- 6.2.2 Measurement Accuracy p. 184
- 6.2.3 Memory Effects in a BJT PA p. 185
- 6.2.4 Memory Effects in an MESFET PA p. 187
- 6.3 Memory Effects and Linearization p. 187

- 6.4 Summary p. 190
- 6.5 Key Points to Remember p. 191
- References p. 192
- Chapter 7 Cancellation of Memory Effects p. 193
- 7.1 Envelope Filtering p. 194
- 7.2 Impedance Optimization p. 198
- 7.2.1 Active Load Principle p. 199
- 7.3 Envelope Injection p. 207
- 7.2.2 Test Setup and Its Calibration p. 202
- 7.2.3 Optimum Z_{BB} at the Envelope Frequency Without Predistortion p. 203
- 7.2.4 Optimum Z_{BB} at the Envelope Frequency with Predistortion p. 204
- 7.3.1 Cancellation of Memory Effects in a CE BJT Amplifier p. 209
- 7.3.2 Cancellation of Memory Effects in a CS MESFET Amplifier p. 211
- 7.4 Summary p. 217
- 7.5 Key Points to Remember p. 219
- References p. 220
- Appendix A Basics of Volterra Analysis p. 221
- Reference p. 225
- Appendix B Truncation Error p. 227
- Appendix C IM3 Equations for Cascaded Second-Degree Nonlinearities p. 231
- Appendix D About the Measurement Setups p. 245
 - Reference p. 247
 - Glossary p. 249
- About the Authors p. 253
- Index p. 255