

Table of Content

Section 1: Electrical Principles

1. International System of Measurement
2. Introduction to Electrical Systems
3. Simple DC Circuits
4. Network Theorems
5. Capacitance and Capacitors
6. Electromagnetism
7. Simple Magnetic Circuits
8. Inductance in a DC Circuit
9. Alternating Voltage and Current
10. Single-phase Series Circuits
11. Single-phase Parallel Networks
12. Power in AC Circuits
13. Complex Notation
14. Resonance in AC Circuits
15. Network Theorems Applied to AC Networks

Section 2: Electronic Engineering

16. Electronic Systems
17. Passive Filters
18. Amplifier Equivalent Networks
19. Semiconductor Materials
20. Rectifiers
21. Junction Transistor Amplifiers
22. FET Amplifiers
23. Further Semiconductor Amplifiers
24. Interfacing Digital and Analogue Systems
25. Digital Numbers
26. Digital Systems
27. Microprocessors and Programs
28. Control Systems
29. Signals
30. Data Transmission and Signals
31. Communications
32. Fibreoptics

Section 3: Power Engineering

33. Multiphase Systems
34. Transformers
35. Introduction to Machine Theory
36. AC Synchronous Machine Windings

- 37. Characteristics of AC Synchronous Machines
- 38. Induction Motors
- 39. Electrical Energy Systems
- 40. Power Systems
- 41. Direct-current Machines
- 42. Direct-current Motors
- 43. Control System Motors
- 44. Motor Selection and Efficiency
- 45. Power Electronics

Section 4: Measurements

- 46. Electronic Measuring Instruments
- 47. Analogue Measuring Instruments