- Preface
- Part I Number Representation
- 1 Numbers and Arithmetic
- 1.1 What is Computer Arithmetic?
- 1.2 A Motivating Example
- 1.3 Numbers and Their Encodings
- 1.4 Fixed-Radix Positional Number Systems
- 1.5 Number Radix Conversion
- 1.6 Classes of Number Representations
- 2 Representing Signed Numbers
- 2.1 Signed-Magnitude Representation
- 2.2 Biased Representations
- 2.3 Complement Representations
- 2.4 Two's- and 1's-Complement Numbers
- 2.5 Direct and Indirect Signed Arithmetic
- 2.6 Using Signed Positions or Signed Digits
- 3 Redundant Number Systems
- 3.1 Coping with the Carry Problem
- 3.2 Redundancy in Computer Arithmetic
- 3.3 Digit Sets and Digit-Set Conversions
- 3.4 Generalized Signed-Digit Numbers
- 3.5 Carry-Free Addition Algorithms
- 3.6 Conversions and Support Functions
- 4 Residue Number Systems
- 4.1 RNS Representation and Arithmetic
- 4.2 Choosing the RNS Moduli
- 4.3 Encoding and Decoding of Numbers
- 4.4 Difficult RNS Arithmetic Operations
- 4.5 Redundant RNS Representations
- 4.6 Limits of Fast Arithmetic in RNS
- Part II Addition/Subtraction
- 5 Basic Addition and Counting
- 5.1 Bit-Serial and Ripple-Carry Adders
- 5.2 Conditions and Exceptions
- 5.3 Analysis of Carry Propagation
- 5.4 Carry Completion Detection
- 5.5 Addition of a Constant: Counters
- 5.6 Manchester Carry Chains and Adders
- 6 Carry-Lookahead Adders
- 6.1 Unrolling the Carry Recurrence
- 6.2 Carry-Lookahead Adder Design
- 6.3 Ling Adder and Related Designs
- 6.4 Carry Determination as Prefix Computation
- 6.5 Alternative Parallel Prefix Networks

- 6.6 VLSI Implementation Aspects
- 7 Variations in Fast Adders
- 7.1 Simple Carry-Skip Adders
- 7.2 Multilevel Carry-Skip Adders
- 7.3 Carry-Select Adders
- 7.4 Conditional-Sum Adder
- 7.5 Hybrid Adder Designs
- 7.6 Optimizations in Fast Adders
- 8 Multi-Operand Addition
- 8.1 Using Two-Operand Adders
- 8.2 Carry-Save Adders
- 8.3 Wallace and Dadda Trees
- 8.4 Parallel Counters
- 8.5 Generalized Parallel Counters
- 8.6 Adding Multiple Signed Numbers
- Part III Multiplication
- 9 Basic Multiplication Schemes
- 9.1 Shift/Add Multiplication Algorithms
- 9.2 Programmed Multiplication
- 9.3 Basic Hardware Multipliers
- 9.4 Multiplication of Signed Numbers
- 9.5 Multiplication by Constants
- 9.6 Preview of Fast Multipliers
- 10 High-Radix Multipliers
- 10.1 Radix-4 Multiplication
- 10.2 Modified Booth's Recoding
- 10.3 Using Carry-Save Adders
- 10.4 Radix-8 and Radix-16 Multipliers
- 10.5 Multibeat Multipliers
- 10.6 VLSI Complexity Issues
- 11 Tree and Array Multipliers
- 11.1 Full Tree Multipliers
- 11.2 Alternative Reduction Trees
- 11.3 Tree Multipliers for Signed Numbers
- 11.4 Partial-Tree Multipliers
- 11.5 Array Multipliers
- 11.6 Pipelined Tree and Array Multipliers
- 12 Variations in Multipliers
- 12.1 Divide-and-Conquer Designs
- 12.2 Additive Multiply Modules
- 12.3 Bit-Serial Multipliers
- 12.4 Modular Multipliers
- 12.5 The Special Case of Squaring
- 12.6 Combined Multiply-Add Units

- Part IV Division
- 13 Basic Divis