

- Preface
- Getting Files from the Wiley ftp and Internet Sites
- Symbols List and Glossary
- 1 Introduction
 - 1.1 System Design Process
 - 1.2 Organization of the Book
 - 1.3 Appendixes
 - 1.4 Spreadsheets
 - 1.5 Test and Simulation
 - 1.6 Practical Skepticism
 - 1.7 References
- 2 Gain
 - 2.1 Simple Cases
 - 2.2 General Case
 - 2.3 Simplification: Unilateral Modules
 - 2.4 Nonstandard Impedances
 - 2.5 Use of Sensitivities to Find Variations
 - 2.6 Summary
 - Endnotes
- 3 Noise Figure
 - 3.1 Noise Factor and Noise Figure
 - 3.2 Modules in Cascade
 - 3.3 Applicable Gains and Noise Factors
 - 3.4 Noise Figure of an Attenuator
 - 3.5 Noise Figure of an Interconnect
 - 3.6 Cascade Noise Figure
 - 3.7 Expected Value and Variance of Noise Figure
 - 3.8 Impedance-Dependent Noise Factors
 - 3.9 Image Noise, Mixer
 - 3.10 Extreme Mismatch, Voltage Amplifiers
 - 3.11 Using Noise Figure Sensitivities
 - 3.12 Mixed Cascade Example
 - 3.13 Gain Controls
 - 3.14 Summary
 - Endnotes
- 4 Nonlinearity in the Signal Path
 - 4.1 Representing Nonlinear Responses
 - 4.2 Second-Order Terms
 - 4.3 Third-Order Terms
 - 4.4 Frequency Dependence and Relationship Between Products
 - 4.5 Nonlinear Products in the Cascades
 - 4.6 Examples: Spreadsheets for IMs in a Cascade
 - 4.7 Anomalous IMs
 - 4.8 Measuring IMs
 - 4.9 Compression in the Cascade
 - 4.10 Other Nonideal Effects

- 4.11 Summary
- Endnote
- 5 Noise and Nonlinearity
- 5.1 Intermodulation of Noise
- 5.2 Composite Distortion
- 5.3 Dynamic Range
- 5.4 Optimizing Cascades
- 6 Architectures that Improve Linearity
- 5.5 Spreadsheet Enhancements
- 5.6 Summary
- Endnotes
- 6.1 Parallel Combining
- 6.2 Feedback
- 6.3 Feedforward
- 6.4 Nonideal Performance
- 6.5 Summary
- Endnotes
- 7 Frequency Conversion
- 7.4 Power Range for Predictable Levels
- 7.1 Basics
- 7.2 Spurious Levels
- 7.3 Two-Signal IMs
- 7.5 Spur Plot, LO Reference
- 7.6 Spur Plot, IF Reference
- 7.7 Shape Factors
- 7.8 Double Conversion
- 7.9 Operating Regions
- 7.10 Examples
- 7.11 Note on Spur Plots Used in This Chapter
- 7.12 Summary
- Endnotes
- 8 Contaminating Signals in Severe Nonlinearities
- 8.1 Decomposition
- 8.2 Hard Limiting
- 8.3 Soft Limiting
- 8.4 Mixers, Through the LO Port
- 8.5 Frequency Dividers
- 8.6 Frequency Multipliers
- 8.7 Summary
- Endnotes
- 9 Phase Noise
- 9.4 Processing Phase Noise in a Cascade
- 9.1 Describing Phase Noise
- 9.2 Adverse Effects of Phase Noise
- 9.3 Sources of Phase Noise
- 9.5 Determining the Effect on Data

- Appendix A OP AMP Noise Factor Calculations
- 9.6 Other Measures of Phase Noise
- 9.7 Summary
- Endnote
- A.1 Invariance When Input Resistor Is Redistributed
- A.2 Effect of Change in Source Resistances
- A.3 Model
- Appendix B Representations of Frequency Bands, if Normalization
- B.1 Passbands
- B.2 Acceptance Bands
- B.3 Filter Asymmetry
- Appendix C Conversion Arithmetic
- C.1 Receiver Calculator
- C.2 Synthesis Calculator
- Appendix E Example of Frequency Conversion
- Appendix F Some Relevant Formulas
- F.1 Decibels
- F.2 Reflection Coefficient and SWR
- F.3 Combining SWRs
- F.3.1 Summary of Results
- F.3.2 Development