

- Part I Power Electronic Devices
- 1 Power Electronics
- 1.1 Overview Kaushik Rajashekara p. 1
- 1.2 Diodes Sohail Anwar p. 1
- 1.3 Schottky Diodes Sohail Anwar p. 1
- 1.4 Thyristors Sohail Anwar p. 1
- 1.5 Power Bipolar Junction Transistors Sohail Anwar p. 1
- 1.6 Mosfets Vrej Barkhordarian p. 1
- 1.7 General Power Semiconductor Switch Requirements Alex Q. Huang p. 1
- 1.8 Gate Turn-Off Thyristors Alex Q. Huang p. 1
- 1.9 Insulated Gate Bipolar Transistors Alex Q. Huang p. 1
- 1.10 Gate-Commutated Thyristors and Other Hard-Driven GTOs Alex Q. Huang p. 1
- 1.11 Comparison Testing of Switches Alex Q. Huang p. 1
- Part II Power Electronic Circuits and Controls
- 2 DC-DC Converters
- 2.1 Overview Richard Wies and Bipin Satavalekar and Ashish Agrawal p. 2
- 2.2 Choppers Javad Mahdavi and Ali Agah and Ali Emadi p. 2
- 2.3 Buck Converters Richard Wies and Bipin Satavalekar and Ashish Agrawal p. 2
- 2.4 Boost Converters Richard Wies and Bipin Satavalekar and Ashish Agrawal p. 2
- 2.5 Cuk Converter Richard Wies and Bipin Satavalekar and Ashish Agrawal p. 2
- 2.6 Buck-Boost Converters Daniel Jeffrey Shortt p. 2
- 3 AC-AC Conversion Sandor Halasz
- 3.1 Introduction p. 3
- 3.2 Cycloconverters p. 3
- 3.3 Matrix Converters p. 3
- 4 Rectifiers
- 4.1 Uncontrolled Single-Phase Rectifiers Sam Guccione p. 4
- 4.2 Uncontrolled and Controlled Rectifiers Mahesh M. Swamy p. 4
- 4.3 Three-Phase Pulse-Width-Modulated Boost-Type Rectifiers Ana Stankovic p. 4
- 5 Inverters
- 5.1 Overview Michael Giesselmann p. 5
- 5.2 DC-AC Conversion Attila Karpati p. 5
- 5.3 Resonant Converters Istvan Nagy p. 5
- 5.4 Series-Resonant Inverters Dariusz Czarkowski p. 5
- 5.5 Resonant DC-Link Inverters Michael B. Ropp p. 5
- 5.6 Auxiliary Resonant Commutated Pole Inverters Eric Walters and Oleg Wasynczuk p. 5
- 6 Multilevel Converters Keith Corzine
- 6.1 Introduction p. 6
- 6.2 Multilevel Voltage Source Modulation p. 6
- 6.3 Fundamental Multilevel Converter Topologies p. 6
- 6.4 Cascaded Multilevel Converter Topologies p. 6
- 6.5 Multilevel Converter Laboratory Examples p. 6
- 6.6 Conclusion p. 6
- 7 Modulation Strategies
- 7.1 Introduction Michael Giesselmann p. 7

- 7.2 Six-Step Modulation Michael Giesselmann p. 7
- 7.3 Pulse Width Modulation Michael Giesselmann p. 7
- 7.4 Third Harmonic Injection for Voltage Boost of SPWM Signals Michael Giesselmann p. 7
- 7.5 Generation of PWM Signals Using Microcontrollers and DSPs Michael Giesselmann p. 7
- 7.6 Voltage-Source-Based Current Regulation Michael Giesselmann p. 7
- 7.7 Hysteresis Feedback Control Hossein Salehfar p. 7
- 7.8 Space-Vector Pulse Width Modulation Hamid A. Toliyat and Tahmid Ur Rahman p. 7
- 8 Sliding-Mode Control of Switched-Mode Power Supplies Giorgio Spiazzi and Paolo Mattavelli
  - 8.1 Introduction p. 8
  - 8.2 Introduction to Sliding-Mode Control p. 8
  - 8.3 Basics of Sliding-Mode Theory p. 8
  - 8.4 Application of Sliding-Mode Control to DC-DC Converters--Basic Principle p. 8
  - 8.5 Sliding-Mode Control of Buck DC-DC Converters p. 8
  - 8.6 Extension to Boost and Buck-Boost DC-DC Converters p. 8
  - 8.7 Extension to Cuk and SEPIC DC-DC Converters p. 8
  - 8.8 General-Purpose Sliding-Mode Control Implementation p. 8
  - 8.9 Conclusions p. 8
- Part III Applications and Systems Considerations
- 9 DC Motor Drives Ralph Staus
  - 9.1 DC Motor Basics p. 9
  - 9.2 DC Speed Control p. 9
  - 9.3 DC Drive Basics p. 9
  - 9.4 Transistor PWM DC Drives p. 9
  - 9.5 SCR DC Drives p. 9
- 10 AC Machines Controlled as DC Machines (Brushless DC Machines/Electronics) Hamid A. Toliyat and Tilak Gopalarathnam
  - 10.1 Introduction p. 10
  - 10.2 Machine Construction p. 10
  - 10.3 Motor Characteristics p. 10
  - 10.4 Power Electronic Converter p. 10
  - 10.5 Position Sensing p. 10
  - 10.6 Pulsating Torque Components p. 10
  - 10.7 Torque-Speed Characteristics p. 10
  - 10.8 Applications p. 10
- 11 Control of Induction Machine Drives Daniel Logue and Philip T. Krein
  - 11.1 Introduction p. 11
  - 11.2 Scalar Induction Machine Control p. 11
  - 11.3 Vector Control of Induction Machines p. 11
  - 11.4 Summary p. 11
- 12 Permanent-Magnet Synchronous Machine Drives Patrick L. Chapman
  - 12.1 Introduction p. 12
  - 12.2 Construction of PMSM Drive Systems p. 12

- 12.3 Simulation and Model p. 12
- 12.4 Controlling the PMSM p. 12
- 12.5 Advanced Topics in PMSM Drives p. 12
- 13 Switched Reluctance Machines Iqbal Husain
- 13.1 Introduction p. 13
- 13.2 SRM Configuration p. 13
- 13.3 Basic Principle of Operation p. 13
- 13.4 Design p. 13
- 13.5 Converter Topologies p. 13
- 13.6 Control Strategies p. 13
- 13.7 Sensorless Control p. 13
- 13.8 Applications p. 13
- 14 Step Motor Drives Ronald H. Brown
- 14.1 Introduction p. 14
- 14.2 Types and Operation of Step Motors p. 14
- 14.3 Step Motor Models p. 14
- 14.4 Control of Step Motors p. 14
- 15 Servo Drives Sandor Halasz
- 15.1 DC Drives p. 15
- 15.2 Induction Motor Drives p. 15
- 16 Uninterruptible Power Supplies Laura Steffek and John Hacklesmiller and Dave Layden and Brian Young
- 16.1 UPS Functions p. 16
- 16.2 Static UPS Topologies p. 16
- 16.3 Rotary UPSs p. 16
- 16.4 Alternate AC and DC Sources p. 16
- 17 Power Quality and Utility Interface Issues
- 17.1 Overview Wayne Galli p. 17
- 17.2 Power Quality Considerations Timothy L. Skvarenina p. 17
- 17.3 Passive Harmonic Filters Badrul H. Chowdhury p. 17
- 17.4 Active Filters for Power Conditioning Hirofumi Akagi p. 17
- 17.5 Unity Power Factor Rectification Rajapandian Ayyanar and Amit Kumar Jain p. 17
- 18 Photovoltaic Cells and Systems Roger Messenger
- 18.1 Introduction p. 18
- 18.2 Solar Cell Fundamentals p. 18
- 18.3 Utility Interactive PV Applications p. 18
- 18.4 Stand-Alone PV Systems p. 18
- 19 Flexible, Reliable, and Intelligent Electrical Energy Delivery Systems Alexander Domijan, Jr. and Zhidong Song
- 19.1 Introduction p. 19
- 19.2 The Concept of FRIENDS p. 19
- 19.3 Development of FRIENDS p. 19
- 19.4 The Advanced Power Electronic Technologies within QCCs p. 19
- 19.5 Significance of FRIENDS p. 19
- 19.6 Realization of FRIENDS p. 19
- 19.7 Conclusions p. 19

- 20 Unified Power Flow Controllers Ali Feliachi and Azra Hasanovic and Karl Schoder
- 20.1 Introduction p. 20
- 20.2 Power Flow on a Transmission Line p. 20
- 20.3 UPFC Description and Operation p. 20
- 20.4 UPFC Modeling p. 20
- 20.5 Control Design p. 20
- 20.6 Case Study p. 20
- 20.7 Conclusion p. 20
- Acknowledgment p. 20
- 21 More-Electric Vehicles Ali Emadi and Mehrdad Ehsani
- 21.1 Aircraft Ali Emadi and Mehrdad Ehsani p. 21
- 21.2 Terrestrial Vehicles Ali Emadi and Mehrdad Ehsani p. 21
- 22 Principles of Magnetics Roman Stempok
- 22.1 Introduction p. 22
- 22.2 Nature of a Magnetic Field p. 22
- 22.3 Electromagnetism p. 22
- 22.4 Magnetic Flux Density p. 22
- 22.5 Magnetic Circuits p. 22
- 22.6 Magnetic Field Intensity p. 22
- 22.7 Maxwell's Equations p. 22
- 22.8 Inductance p. 22
- 22.9 Practical Considerations p. 22
- 23 Computer Simulation of Power Electronics Michael Giesselmann
- 23.1 Introduction p. 23
- 23.2 Code Qualification and Model Validation p. 23
- 23.3 Basic Concepts--Simulation of a Buck Converter p. 23
- 23.4 Advanced Techniques--Simulation of a Full-Bridge (H-Bridge) Converter p. 23
- 23.5 Conclusions p. 23
- Index p. I