

- Preface p. ix
- 1 Introduction p. 1
- 1.1 Microwave Transmission Lines p. 4
- 1.2 Transmitter and Receiver Architectures p. 8
- 2 Communication Systems p. 11
- 2.1 Terrestrial Communication p. 12
- 2.2 Satellite Communication p. 13
- 2.3 Radio-Frequency Wireless Services p. 16
- 2.4 Antenna Systems p. 18
- 2.5 Noise and Distortion p. 33
- Suggested Reading p. 52
- Problems p. 52
- 3 Transmission Lines p. 57
- 3.1 Distributed Circuit Analysis of Transmission Lines p. 57
- 3.2 Sending-End Impedance p. 67
- 3.3 Standing Wave and Standing Wave Ratio p. 80
- 3.4 Smith Chart p. 85
- Suggested Reading p. 95
- Problems p. 95
- 4 Electromagnetic Fields and Waves p. 104
- 4.1 Fundamental Laws of Electromagnetic Fields p. 104
- 4.2 The Wave Equation and Uniform Plane Wave Solutions p. 114
- 4.3 Boundary Conditions p. 119
- 4.4 Uniform Plane Wave Incident Normally on an Interface p. 123
- 4.5 Modified Maxwell's Equations and Potential Functions p. 126
- 4.6 Construction of Solutions p. 130
- 4.7 Metallic Parallel-Plate Waveguide p. 133
- 4.8 Metallic Rectangular Waveguide p. 137
- 4.9 Metallic Circular Waveguide p. 142
- Suggested Reading p. 145
- Problems p. 145
- 5 Resonant Circuits p. 151
- 5.1 Series Resonant Circuits p. 151
- 5.2 Parallel Resonant Circuits p. 160
- 5.3 Transformer-Coupled Circuits p. 164
- 5.4 Transmission Line Resonant Circuits p. 170
- 5.5 Microwave Resonators p. 177
- Suggested Reading p. 184
- Problems p. 184
- 6 Impedance-Matching Networks p. 189
- 6.1 Single Reactive Element or Stub Matching Networks p. 190
- 6.2 Double-Stub Matching Networks p. 202
- 6.3 Matching Networks Using Lumped Elements p. 207
- Suggested Reading p. 226
- Problems p. 226
- 7 Impedance Transformers p. 234

- 7.1 Single-Section Quarter-Wave Transformers p. 234
- 7.2 Multisection Quarter-Wave Transformers p. 237
- 7.3 Transformer with Uniformly Distributed Section Reflection Coefficients p. 239
- 7.4 Binomial Transformers p. 244
- 7.5 Chebyshev Transformers p. 248
- 7.6 Exact Formulation and Design of Multisection Impedance Transformers p. 255
- 7.7 Tapered Transmission Lines p. 263
- 7.8 Synthesis of Transmission Line Tapers p. 270
- 7.9 Bode-Fano Constraints for Lossless Matching Networks p. 280
- Suggested Reading p. 281
- Problems p. 281
- 8 Two-Port Networks p. 283
- 8.1 Impedance Parameters p. 284
- 8.2 Admittance Parameters p. 289
- 8.3 Hybrid Parameters p. 296
- 8.4 Transmission Parameters p. 298
- 8.5 Conversion of Impedance, Admittance, Chain, and Hybrid Parameters p. 304
- 8.6 Scattering Parameters p. 304
- 8.7 Conversion From Impedance, Admittance, Chain, and Hybrid Parameters to Scattering Parameters, or Vice Versa p. 323
- 8.8 Chain Scattering Parameters p. 325
- Suggested Reading p. 325
- Problems p. 326
- 9 Filter Design p. 333
- 9.1 Image Parameter Method p. 334
- 9.2 Insertion-Loss Method p. 353
- 9.3 Microwave Filters p. 380
- Suggested Reading p. 389
- Problems p. 389
- 10 Signal-Flow Graphs and Their Applications p. 392
- 10.1 Definitions and Manipulation of Signal-Flow Graphs p. 396
- 10.2 Signal-Flow Graph Representation of a Voltage Source p. 401
- 10.3 Signal-Flow Graph Representation of a Passive Single-Port Device p. 402
- 10.4 Power Gain Equations p. 410
- Suggested Reading p. 417
- Problems p. 418
- 11 Transistor Amplifier Design p. 422
- 11.1 Stability Considerations p. 422
- 11.2 Amplifier Design for Maximum Gain p. 429
- 11.3 Constant-Gain Circles p. 439
- 11.4 Constant Noise Figure Circles p. 457
- 11.5 Broadband Amplifiers p. 466
- 11.6 Small-Signal Equivalent-Circuit Models of Transistors p. 469
- 11.7 DC Bias Circuits for Transistors p. 472
- Suggested Reading p. 475
- Problems p. 476

- 12 Oscillator Design p. 479
- 12.1 Feedback and Basic Concepts p. 479
- 12.2 Crystal Oscillators p. 492
- 12.3 Electronic Tuning of Oscillators p. 494
- 12.4 Phase-Locked Loop p. 497
- 12.5 Frequency Synthesizers p. 516
- 12.6 One-Port Negative Resistance Oscillators p. 520
- 12.7 Microwave Transistor Oscillators p. 523
- Suggested Reading p. 538
- Problems p. 538
- 13 Detectors and Mixers p. 543
- 13.1 Amplitude Modulation p. 544
- 13.2 Frequency Modulation p. 555
- 13.3 Switching-Type Mixers p. 559
- 13.4 Conversion Loss p. 565
- 13.5 Intermodulation Distortion in Diode-Ring Mixers p. 567
- 13.6 FET Mixers p. 571
- Suggested Reading p. 577
- Problems p. 577
- Appendix 1 Decibels and Neper p. 580
- Appendix 2 Characteristics of Selected Transmission Lines p. 582
- Appendix 3 Specifications of Selected Coaxial Lines and Waveguides p. 588
- Appendix 4 Some Mathematical Formulas p. 590
- Appendix 5 Vector Identities p. 593
- Appendix 6 Some Useful Network Transformations p. 596
- Appendix 7 Properties of Some Materials p. 599
- Appendix 8 Common Abbreviations p. 601
- Appendix 9 Physical Constants p. 609
- Index p. 611