

Contents

1

REVIEW OF ELECTROMAGNETIC THEORY 1

- 1.1 Introduction to Microwave Engineering 1**
 - Applications of Microwave Engineering 2
 - A Short History of Microwave Engineering 6
 - Electromagnetic Compatibility and Electromagnetic Interference 6
- 1.2 Maxwell's Equations 7**
- 1.3 Fields in Media and Boundary Conditions 11**
 - Fields at a General Material Interface 13
 - Fields at a Dielectric Interface 14
 - Fields at the Interface with a Perfect Conductor (Electric Wall) 14
 - The Magnetic Wall Boundary Condition 15
 - The Radiation Condition 15
- 1.4 The Wave Equation and Basic Plane Wave Solutions 15**
 - The Helmholtz Equation 15
 - Plane Waves in a Lossless Medium 16
 - Plane Waves in a General Lossy Medium 17
 - Plane Waves in a Good Conductor 18
- 1.5 General Plane Wave Solutions 20**
 - Circularly Polarized Plane Waves 23
- 1.6 Energy and Power 24**
 - Power Absorbed by a Good Conductor 25
- 1.7 Plane Wave Reflection from a Media Interface 27**
 - General Medium 27
 - Lossless Medium 28
 - Good Conductor 30
 - Perfect Conductor 31
 - The Surface Impedance Concept 31

1.8 Oblique Incidence at a Dielectric Interface 33

- Parallel Polarization 34
- Perpendicular Polarization 35
- Total Reflection and Surface Waves 37

1.9 Some Useful Theorems 38

- The Reciprocity Theorem 38
- Image Theory 39

2

TRANSMISSION LINE THEORY 47

2.1 The Lumped-Element Circuit Model for a Transmission Line 47

- Wave Propagation on a Transmission Line 48
- The Lossless Line 49

2.2 Field Analysis of Transmission Lines 50

- Transmission Line Parameters 50
- The Telegrapher Equations Derived from Field Analysis of a Coaxial Line 52
- Propagation Constant, Impedance, and Power Flow for the Lossless Coaxial Line 53

2.3 The Terminated Lossless Transmission Line 54

- Special Cases of Lossless Terminated Lines 57

2.4 The Smith Chart 60

- The Combined Impedance–Admittance Smith Chart 63
- The Slotted Line 65
- Online Smith Chart 68

2.5 Generator and Load Mismatches 68

- Load Matched to Line 70
- Generator Matched to Loaded Line 70
- Conjugate Matching 70

2.6 Lossy Transmission Lines 72

- The Low-Loss Line 72
- The Distortionless Line 73

The Terminated Lossy Line 74
 The Perturbation Method for Calculating Attenuation 74
 The Wheeler Incremental Inductance Rule 76

2.7 Transients on Transmission Lines 78

Reflection of Pulses from a Terminated Transmission Line 78
 Bounce Diagrams for Transient Propagation 80

3 TRANSMISSION LINES AND WAVEGUIDES 87

3.1 General Solutions for TEM, TE, and TM Waves 88

TEM Waves 89
 Impossibility of TEM Mode 91
 TE Waves 91
 TM Waves 92
 Attenuation Due to Dielectric Loss 92

3.2 Parallel Plate Waveguide 93

TEM Modes 93
 TM Modes 95
 TE Modes 98

3.3 Rectangular Waveguide 101

TE Modes 101
 TM Modes 105
 TE_{m0} Modes of a Partially Loaded Waveguide 109

3.4 Circular Waveguide 112

TE Modes 113
 TM Modes 116

3.5 Coaxial Line 121

TEM Modes 121
 Higher Order Modes 122

3.6 Surface Waves on a Grounded Dielectric Sheet 125

TM Modes 125
 TE Modes 127

3.7 Stripline 130

Formulas for Propagation Constant, Characteristic Impedance, and Attenuation 132
 An Approximate Electrostatic Solution 134

3.8 Microstrip Line 136

Formulas for Effective Dielectric Constant, Characteristic Impedance, and Attenuation 137
 Frequency-Dependent Effects and Higher Order Modes 139

3.9 The Transverse Resonance Technique 141

TE_{0n} Modes of a Partially Loaded Rectangular Waveguide 142

3.10 Wave Velocities and Dispersion 143

Group Velocity 143

3.11 Summary of Transmission Lines and Waveguides 145

Other Types of Lines and Guides 146

4 MICROWAVE NETWORK ANALYSIS 153

4.1 Impedance and Equivalent Voltages and Currents 154

Equivalent Voltages and Currents 154
 The Concept of Impedance 157
 Even and Odd Properties of $Z(\omega)$ and $\Gamma(\omega)$ 159

4.2 Impedance and Admittance Matrices 160

Reciprocal Networks 162
 Lossless Networks 163

4.3 The Scattering Matrix 164

Reciprocal Networks and Lossless Networks 167
 A Shift in Reference Planes 169
 Power Waves and Generalized Scattering Parameters 171

4.4 The Transmission ($ABCD$) Matrix 174

Relation to Impedance Matrix 175
 Equivalent Circuits for Two-Port Networks 177

4.5 Signal Flow Graphs 177

Decomposition of Signal Flow Graphs 180
 Application to Thru-Reflect-Line Network Analyzer Calibration 183

4.6 Discontinuities and Modal Analysis 187

Modal Analysis of an H -Plane Step in Rectangular Waveguide 187

- 4.7 Excitation of Waveguides—Electric and Magnetic Currents 193**
 Current Sheets That Excite Only One Waveguide Mode 193
 Mode Excitation from an Arbitrary Electric or Magnetic Current Source 195
- 5 IMPEDANCE MATCHING AND TUNING 204**
- 5.1 Matching with Lumped Elements (L Networks) 205**
 Analytical Solutions 205
 Smith Chart Solutions 206
- 5.2 Single-Stub Tuning 209**
 Shunt Stubs 210
 Series Stubs 213
- 5.3 Double-Stub Tuning 216**
 Smith Chart Solution 216
 Analytical Solution 219
- 5.4 The Quarter-Wave Transformer 220**
 The Impedance Viewpoint 220
 The Multiple-Reflection Viewpoint 222
 Impedance Matching of the Quarter-Wave Transformer 223
- 5.5 The Theory of Small Reflections 226**
 Single-Section Transformer 226
 Multisection Transformer 228
- 5.6 Binomial Multisection Matching Transformers 228**
- 5.7 Chebyshev Multisection Matching Transformers 232**
 Chebyshev Polynomials 232
 Design of Chebyshev Transformers 233
- 5.8 Tapered Lines 236**
 Exponential Taper 237
 Triangular Taper 238
 Klopfenstein Taper 238
- 6 MICROWAVE RESONATORS 244**
- 6.1 Series and Parallel Resonant Circuits 244**
 Series Resonant Circuit 244
 Parallel Resonant Circuit 247
 Loaded and Unloaded Q 249
- 6.2 Transmission Line Resonators 249**
 Short-Circuited $\lambda/2$ Line 250
 Short-Circuited $\lambda/4$ Line 252
 Open-Circuited $\lambda/2$ Line 252
- 6.3 Rectangular Waveguide Cavity Resonators 254**
 Resonant Frequencies 254
 Unloaded Q of the $TE_{10\ell}$ Mode 256
- 6.4 Circular Waveguide Cavity Resonators 258**
 Resonant Frequencies 258
 Unloaded Q of the $TE_{nm\ell}$ Mode 260
- 6.5 Dielectric Resonators 263**
 Resonant Frequencies of $TE_{01\delta}$ Mode 263
- 6.6 Excitation of Resonators 266**
 The Coupling Coefficient and Critical Coupling 266
 A Gap-Coupled Microstrip Resonator 268
- 7 POWER DIVIDERS AND DIRECTIONAL COUPLERS 275**
- 7.1 Basic Properties of Dividers and Couplers 275**
 Three-Port Networks (T-Junctions) 275
 Four-Port Networks (Directional Couplers) 278
- 7.2 The T-Junction Power Divider 282**
 Lossless Divider 282
 Resistive Divider 284
- 7.3 The Wilkinson Power Divider 285**
 Even-Odd Mode Analysis 285
 Unequal Power Division and N -Way Wilkinson Dividers 288
- 7.4 Waveguide Directional Couplers 290**
 Bethe Hole Coupler 290
 Design of Multihole Couplers 294
- 7.5 The Quadrature (90°) Hybrid 298**
 Even-Odd Mode Analysis 299
- 7.6 Coupled Line Directional Couplers 302**
 Coupled Line Theory 302
 Design of Coupled Line Couplers 306
 Design of Multisection Coupled Line Couplers 310

- 7.7 The Lange Coupler 313
- 7.8 The 180° Hybrid 316
 - Even-Odd Mode Analysis of the Ring Hybrid 318
 - Even-Odd Mode Analysis of the Tapered Coupled Line Hybrid 321
 - Waveguide Magic-T 324
- 7.9 Other Couplers 325

8 MICROWAVE FILTERS 333

- 8.1 Periodic Structures 334
 - Analysis of Infinite Periodic Structures 334
 - Terminated Periodic Structures 336
 - k - β Diagrams and Wave Velocities 337
- 8.2 Filter Design by the Image Parameter Method 340
 - Image Impedances and Transfer Functions for Two-Port Networks 340
 - Constant- k Filter Sections 342
 - m -Derived Filter Sections 344
 - Composite Filters 347
- 8.3 Filter Design by the Insertion Loss Method 349
 - Characterization by Power Loss Ratio 350
 - Maximally Flat Low-Pass Filter Prototype 352
 - Equal-Ripple Low-Pass Filter Prototype 355
 - Linear Phase Low-Pass Filter Prototypes 355
- 8.4 Filter Transformations 355
 - Impedance and Frequency Scaling 356
 - Bandpass and Bandstop Transformations 361
- 8.5 Filter Implementation 364
 - Richards' Transformation 364
 - Kuroda's Identities 364
 - Impedance and Admittance Inverters 369
- 8.6 Stepped-Impedance Low-Pass Filters 370
 - Approximate Equivalent Circuits for Short Transmission Line Sections 370

- Comparison of Richards' Transformation and Stepped-Impedance Method 373

- 8.7 Coupled Line Filters 373
 - Filter Properties of a Coupled Line Section 374
 - Design of Coupled Line Bandpass Filters 377

9 THEORY AND DESIGN OF FERRIMAGNETIC COMPONENTS 387

- 9.1 Basic Properties of Ferrimagnetic Materials 388
 - The Permeability Tensor 388
 - Circularly Polarized Fields 392
 - Effect of Loss 394
 - Demagnetization Factors 396
- 9.2 Plane Wave Propagation in a Ferrite Medium 399
 - Propagation in Direction of Bias (Faraday Rotation) 399
 - Propagation Transverse to Bias (Birefringence) 402
- 9.3 Propagation in a Ferrite-Loaded Rectangular Waveguide 404
 - TE_{m0} Modes of Waveguide with a Single Ferrite Slab 404
 - TE_{m0} Modes of Waveguide with Two Symmetric Ferrite Slabs 407
- 9.4 Ferrite Isolators 408
 - Resonance Isolators 409
 - The Field Displacement Isolator 411
- 9.5 Ferrite Phase Shifters 413
 - Nonreciprocal Latching Phase Shifter 414
 - Other Types of Ferrite Phase Shifters 416
 - The Gyration 417
- 9.6 Ferrite Circulators 418
 - Properties of a Mismatched Circulator 418
 - Junction Circulator 419

10 NOISE AND NONLINEAR DISTORTION 427

- 10.1 Noise in Microwave Circuits 427
 - Dynamic Range and Sources of Noise 427

Noise Power and Equivalent Noise Temperature 429
 Measurement of Noise Temperature 431

10.2 Noise Figure 432

Definition of Noise Figure 432
 Noise Figure of a Cascaded System 434
 Noise Figure of a Passive Two-Port Network 436
 Noise Figure of a Mismatched Lossy Line 437
 Noise Figure of a Mismatched Amplifier 439

10.3 Nonlinear Distortion 440

Gain Compression 441
 Harmonic and Intermodulation Distortion 442
 Third-Order Intercept Point 443
 Intercept Point of a Cascaded System 444
 Passive Intermodulation 446

10.4 Dynamic Range 447

Linear and Spurious Free Dynamic Range 447

11 ACTIVE RF AND MICROWAVE DEVICES 453

11.1 Diodes and Diode Circuits 453

Schottky Diodes and Detectors 454
 PIN Diodes and Control Circuits 458
 Varactor Diodes 464
 Ridley–Watkins–Hilsum (RWH) Theory 465
 Two-Valley Model Theory 465
 Other Diodes 467
 Power Combining 468

11.2 Bipolar Junction Transistors 469

Bipolar Junction Transistor 469
 Heterojunction Bipolar Transistor 470

11.3 Field Effect Transistors 471

Metal Semiconductor Field Effect Transistor 472
 Metal Oxide Semiconductor Field Effect Transistor 473
 High Electron Mobility Transistor 474

11.4 Microwave Integrated Circuits 475

Hybrid Microwave Integrated Circuits 475

Monolithic Microwave Integrated Circuits 476

11.5 Microwave Tubes 479

Klystron 480
 Traveling Wave Tube 482
 Backward Wave Oscillator 482
 Extended Interaction Oscillator 483
 Magnetrons 483
 Cross-Field Amplifier 483
 Gyatron 483

12 MICROWAVE AMPLIFIER DESIGN 487

12.1 Two-Port Power Gains 487

Definitions of Two-Port Power Gains 487
 Further Discussion of Two-Port Power Gains 491

12.2 Stability 492

Stability Circles 493
 Tests for Unconditional Stability 495

12.3 Single-Stage Transistor Amplifier Design 498

Design for Maximum Gain (Conjugate Matching) 498
 Constant-Gain Circles and Design for Specified Gain 503
 Low-Noise Amplifier Design 506
 Low-Noise MOSFET Amplifier 510

12.4 Broadband Transistor Amplifier Design 511

Balanced Amplifiers 512
 Distributed Amplifiers 514
 Differential Amplifiers 518

12.5 Power Amplifiers 521

Characteristics of Power Amplifiers and Amplifier Classes 521
 Large-Signal Characterization of Transistors 522
 Design of Class A Power Amplifiers 523

13 OSCILLATORS AND MIXERS 529

13.1 RF Oscillators 530

General Analysis 530
 Oscillators Using a Common Emitter BJT 531
 Oscillators Using a Common Gate FET 533

Practical Considerations	534
Crystal Oscillators	535
13.2 Microwave Oscillators	536
Transistor Oscillators	538
Dielectric Resonator Oscillators	541
13.3 Oscillator Phase Noise	544
Representation of Phase Noise	544
Leeson's Model for Oscillator Phase Noise	545
13.4 Frequency Multipliers	549
Reactive Diode Multipliers (Manley–Rowe Relations)	549
Resistive Diode Multipliers	552
Transistor Multipliers	553
13.5 Mixers	557
Mixer Characteristics	557
Single-Ended Diode Mixer	561
Single-Ended FET Mixer	562
Balanced Mixer	564
Image Reject Mixer	567
Differential FET Mixer and Gilbert Cell Mixer	568
Other Mixers	570

14 INTRODUCTION TO MICROWAVE SYSTEMS 576

14.1 System Aspects of Antennas	576
Fields and Power Radiated by an Antenna	579
Antenna Pattern Characteristics	580
Antenna Gain and Efficiency	582
Aperture Efficiency and Effective Area	583
Background and Brightness Temperature	583
Antenna Noise Temperature and G/T	586
14.2 Wireless Communication	588
The Friis Formula	589
Link Budget and Link Margin	590
Radio Receiver Architectures	592
Noise Characterization of a Receiver	594
Digital Modulation and Bit Error Rate	597
Wireless Communication Systems	599

14.3 Radar Systems	603
The Radar Equation	604
Pulse Radar	606
Doppler Radar	607
Radar Cross Section	608
14.4 Radiometer Systems	609
Theory and Applications of Radiometry	609
Total Power Radiometer	611
The Dicke Radiometer	612
14.5 Microwave Propagation	613
Atmospheric Effects	614
Ground Effects	615
Plasma Effects	616
14.6 Other Applications and Topics	616
Microwave Heating	616
Power Transfer	617
Biological Effects and Safety	618

APPENDICES 624

A Prefixes	625
B Vector Analysis	625
C Bessel Functions	627
D Useful Results	629
E Other Mathematical Results	631
F Physical Constants	631
G Conductivities for Some Materials	632
H Dielectric Constants and Loss Tangents for Some Materials	632
I Properties of Some Microwave Ferrite Materials	633
J Standard Rectangular Waveguide Data	633
K Standard Coaxial Cable Data	634

ANSWERS TO SELECTED PROBLEMS 635

INDEX 637